

Electronic Devices

Homework # 1 Solution

March 2020

Question 1. (20 pts)

- a. The amplifier can be used as a linear amplifier for input swing: $L-/A_v \leq v_i \leq L+/A_v$. The input must be used is $3\sin(\omega t)$ [mV]. (10 pts)
- b.

We have:

$$v_o = A_{vo} v_i \frac{R_L}{R_L + R_o} \quad (1)$$

Substitute $v_o = 200 \text{ mV}$ and $R_L = 1 \text{ k}\Omega$ to (1):

$$A_{vo} v_i \frac{1000}{1000 + R_o} = 0.2 \quad (2) \quad (5\text{pts})$$

If $R_L = \infty$, based on (1) and (2), we have:

$$v_o = A_{vo} v_i = \frac{0.2 \times (1000 + R_o)}{1000} = \frac{0.2 \times (1000 + 50)}{1000} \Leftrightarrow v_o = 0.21 \text{ V} \quad (5\text{pts})$$

Question 2: (30pts)

- a.

$$A_v = 100 \times \frac{1}{\left(1 + \frac{jf}{10^5}\right)} \times \frac{1}{\left(1 + \frac{10^2}{jf}\right)}$$

The transfer function is a result of STC low pass and high pass circuit with a gain of 100

- The high pass circuit transfer function is:

$$\frac{1}{\left(1 + \frac{10^2}{jf}\right)}$$

The first cutoff frequency is $f_0 = 10^2 \text{ Hz}$

- The low pass circuit transfer function is:

$$\frac{1}{\left(1 + \frac{jf}{10^5}\right)}$$

The second cutoff frequency is $f_1 = 10^5 \text{ Hz}$

(5 pts)

- The magnitude of A_v

$$|A_v| = 100 \times \frac{1}{\sqrt{1 + \frac{f^2}{10^{10}}}} \times \frac{1}{\sqrt{1 + \frac{10^4}{f^2}}}$$

Then

$$f = 10^2 \rightarrow |A_v| = 70.71$$

$$f = 10^5 \rightarrow |A_v| = 70.39.$$

(5 pts)

- (b) Bode Plot of bandpass response has correct axis-names, units, 3dB frequency and slopes (10pts)
- (c) Bandwidth of this bandpass amplifier is the frequency range between the two cutoff frequencies

$$BW = f_1 - f_0 = 10^5 - 10^2 = 99900 \text{ (Hz)} = 99.9 \text{ (kHz)} \quad (10\text{pts})$$

Question 3: Band Pass Filter (20 pts)


- a.
- The input resistance is 100Ω

$$R_i = \frac{v_i}{i} = R_1 = 100 \Omega$$

- The inverting amplifier has a close-loop gain of -100 V/V

$$G = -\frac{R_2}{R_1} = -100 \Leftrightarrow R_2 = 100R_1 = 10 \text{ k}\Omega \quad (5\text{pts})$$

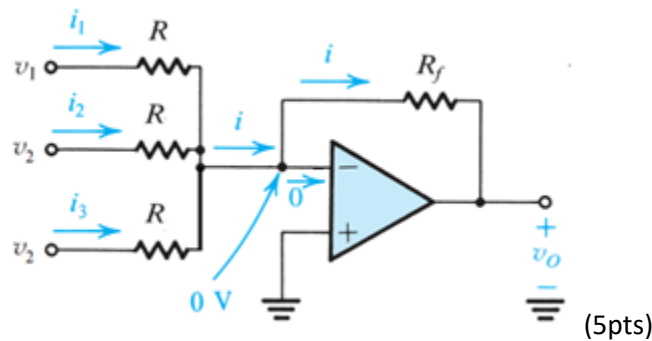- Draw correct inverting amplifier circuit (5pts)
- b.



(5pts)

- $R = 1 \text{ k}\Omega$ and $R_f = 5 \text{ k}\Omega$ are given

$$v_0 = -\left(\frac{R_f}{R}v_1 + \frac{R_f}{R}v_2 + \frac{R_f}{R}v_2\right) = -\left(2 \times \frac{5}{1}v_2 + \frac{5}{1}v_1\right)$$

$$\Leftrightarrow v_0 = -10v_2 - 5v_1 \quad (1)$$

- Substitute $v_1 = 1 \text{ V}$ and $v_2 = -1 \text{ V}$ to (1)

$$v_0 = 5 \text{ V} \quad (5\text{pts})$$

Problem 4: (10 pts)

- Differential input $R_i = 10\text{ k}\Omega = 2R_1 \rightarrow R_1 = 5\text{ k}\Omega = R_3$ (5pts)
- Differential voltage gain: $A_d = \frac{R_2}{R_1} = 50 \rightarrow R_2 = 50R_1 = 250\text{ k}\Omega = R_4$ (5pts)

Problem 5: (20 pts)

- a.
- Inverting amplifier: $\frac{v_o}{v_i} = -\frac{R}{R_f + \frac{1}{j\omega C}} = \frac{-\frac{R}{R_f}}{1 - \frac{j}{\omega C R_f}}$ (5pts)
- High pass network: $\omega_{3dB} = 2\pi f_{3dB} = \frac{1}{C R_f} \rightarrow f_{3dB} = \frac{1}{2\pi C R_f}$ (5pts)
- b.
- $R_{in} = R_f = 1\text{ k}\Omega$.
- $f_{3dB} = 2\text{ kHz} \rightarrow C = \frac{1}{2\pi * 2000 * R_f} = 79.5\text{ nF}$.
- Gain of 20 dB
- $\frac{R}{R_f} = 10^{20/20} = 10 \rightarrow R = 10R_f = 10\text{ k}\Omega$ (5pts)
- Bode Plot has correct axis-names, units, 3dB frequency (5pts)