
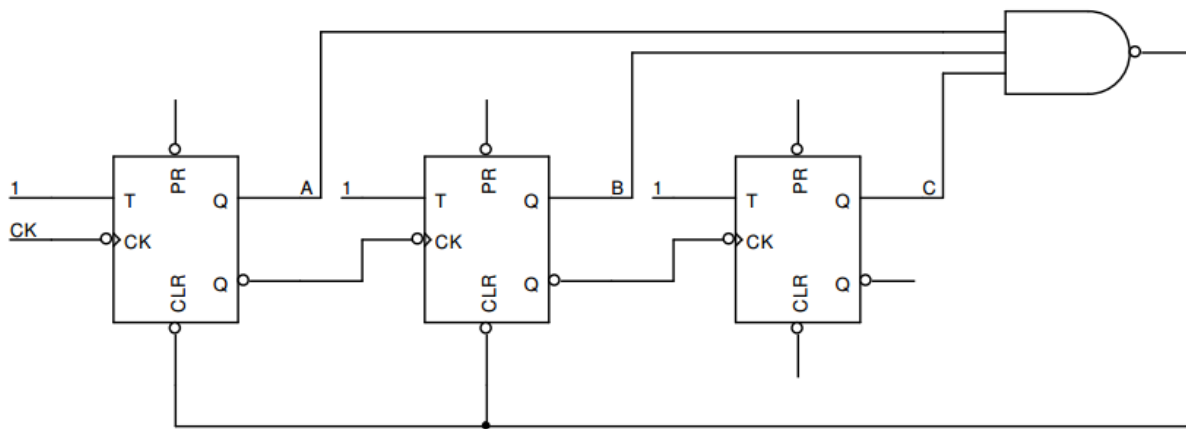


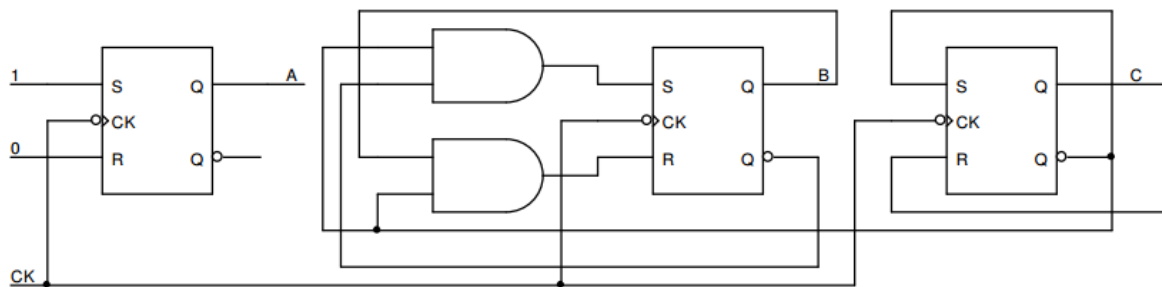1. Analyze the given counter and plot the wave form depend on CLOCK pulse (at least 8 CLOCK pulse).




2. Build the excitation and plot the state diagram of the counter below.



Is this circuit being able to self-working?

3. Give the logic circuit below:

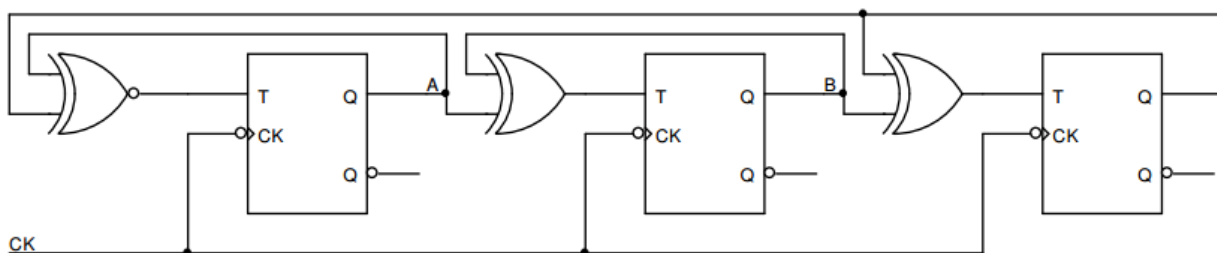

- Implement input function for each FF.
- Describe how the circuit works?

4. The function  $F$  has 4 variables  $A, B, C, D$ . The value of  $F$  is 1 if the decimal value of variables divides 3 or 5 without remainder, otherwise  $F = 0$ .

- a) Implement  $F$  by using 2-input logic gate.
- b) Implement  $F$  by using a MUX 8 to 1 and logic gates (if necessary).
- c) Implement  $F$  by using a MUX 4 to 1 and logic gates (if necessary).
- d) Simplify  $F$  and implement  $F$  using the Half-Adders.

5. Design a logic circuit that counting depend on input control  $P$ . If  $P = 1$  the circuit count  $0 \rightarrow 1 \rightarrow 3 \rightarrow 5 \rightarrow 7 \rightarrow 1$  and when  $P = 0$  the circuit count  $0 \rightarrow 2 \rightarrow 4 \rightarrow 6 \rightarrow 2$ .

- a) Using JK FF.
- b) Using T FF.