

DIGITAL LOGIC DESIGN

Fall 2018

Homework #2


IMPORTANT: This assignment should be done individually. Marks will be deducted if there are sign of violation of regulation and late submission.

Tip: You should draw a bounding box for your final answer. Ex in below:

$$Y = ABC + AC = \boxed{ABC}$$

 Problem 1:


The multiplexer is a logic circuit designed in order to turn one of several input lines to a single common output line. The following figure is a 2 inputs multiplexer which has X and Y input signals. In case that Y is selected when the control input $C = 1$ and X is selected when $C = 0$.



- (a) Create a truth table for the given multiplexer (X and Y are logical variables).
- (b) Write an expression for Z in form of Sum-of-Product.
- (c) Simplify the expression in Part (b) by using K-map.
- (d) Design a logical circuit for Z using 2-inputs NOR gates.

 Problem 2:


The figure below shows a LED display panel which has four light bar A , B , C and D . Design a logic circuit displaying the F letter and L letter using the panel.




- Create a truth table for the design.
- Write an expression for **F** and **L** letter.
- Draw logic circuit for **F** and **L** letters using 2-input NOR gates.
- List other English letters could be shown in this LED panel.

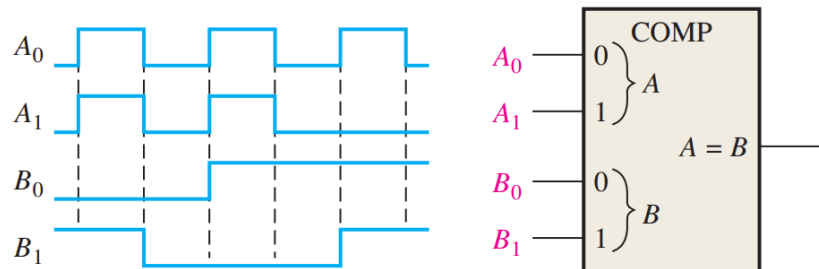Problem 3:

- The given waveforms (blue) are going in the comparator as shown in the following figure. Determine the output waveform from the given input waveform.



- A half-subtractor module has input x , y and output $Diff$, B_{out} (in the figure below). The module subtracts the bits $x - y$ and places the difference in $Diff$ and the borrow in B_{out} . Create a truth table and write the expression for $Diff$ and B_{out} . (Hint: You also can refer the adder).

 

Problem 4:

Implement the following Boolean function with a multiplexer

(a) $F = \Sigma (0, 2, 5, 7, 11, 14)$

(b) $F = \Pi (3, 8, 12)$


Problem 5:

A jet aircraft employs a system for monitoring the rpm, pressure and temperature values of its engines using sensors that operate as follows.

- RPM sensor output = 0 only when speed < 4800 rpm
- P sensor output = 0 only when pressure < 220 psi
- T sensor output = 0 only when temperature < 200°F


For the combinational circuit shown:

- (a) Identify the engine conditions that will give warning to the pilot. Write down the expression
- (b) Using NAND gates only for the expression . Why are NAND and NOR gates called universal gates?

 

 Problem 6:

In a 7-segment display, each of the seven segments is activated for various digits. For instance, segment *a* is activated for the digits 0, 2, 3, 5, 6, 7, 8, and 9, as shown in the following figure. Each digit can be represented by a BCD code.



(a) Write a Sum-of-Product expression for segment *a* using the variables ABCD.


(b) Simplify the expression using K map.

(Hints: In the BCD code, there are six invalid combinations: 1010, 1011, 1100, 1101, 1110, and 1111.


Since these states will never occur in the BCD code, they can be treated as “don’t care” terms which can be noted by ‘x’ in K-map)

Problem 7:

 (a) A D flip-flop is shown in the following figure. Find the Q output in relation to the clock. What function does this circuit perform?



(b) In the figure below, draw a timing diagram for 8 clock pulses for the Q_A and Q_B outputs in given clock.

 


Problem 8:

Design a counter which has the following counting sequence: 0-1-2-3-4 and repeat, 5-0, 6-0, and 7-0. This counter should be designed using D-FFs only.

 Problem 9:

A state transition diagram of a synchronous counter is considered as below Figure. Given that the logical design of this counter consists of **J-K** FF only.




(a) Show the Transition table of this counter.

(b) Find the simplified expressions for each J-K input.

 Problem 10:

A state transition diagram is considered in the figure below



In this figure, E is an enable control input. This input has two states: 0 and 1. Each state of E indicates one separate operation of the state machine given in Figure J-K FFs are considered.

- (a) Derive the logic expressions for each input of FF.
- (b) Modify the circuit in (a) such that at $E = 0$, the state transition machine follows the new sequence: 0-3-2-1-0 and repeat while at $E = 1$, the new sequence is 0-1-2-3-2-0 and repeat. Sketch the new logic circuit.