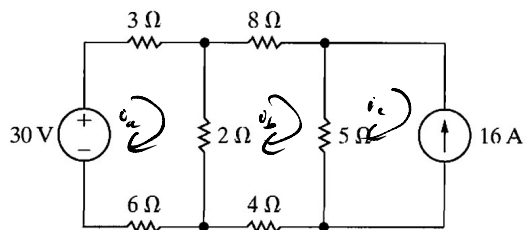





**4.10** Use the mesh-current method to find the power dissipated in the  $2\ \Omega$  resistor in the circuit shown.

**Answer:** 72 W.



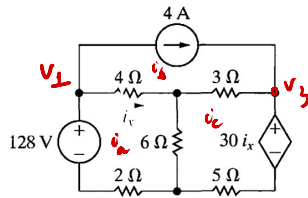4.14 Find the power delivered by the 4 A current source in the circuit shown.



Answer: 40 W.

$$i_b = 4A$$

$$\text{Mesh a: } 4(i_a - i_b) + 6(i_a - i_c) + 2i_a = 128$$

$$\Rightarrow 12i_a - 6i_c = 144$$


$$i_x = i_a - 4 \Rightarrow 30i_x = 30i_a - 120$$

$$\text{Mesh c: } 6(i_c - i_a) + 3(i_c - 4) + 30i_x - 120 + 5i_c = 0$$

$$\Rightarrow 24i_a + 14i_c = 132$$

$$\Rightarrow \begin{cases} i_a = 9 \\ i_c = -6 \end{cases}$$




KVL outer loop

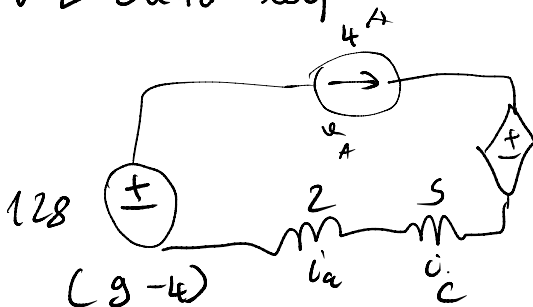


$$v_{4A} + 30i_x + 5i_c + 2i_a - 128 = 0$$

$$\Rightarrow v_{4A} = -10V \rightarrow P = (-10)4 = -40$$

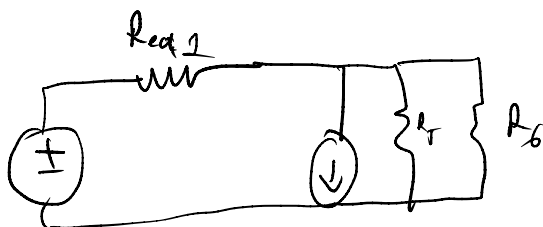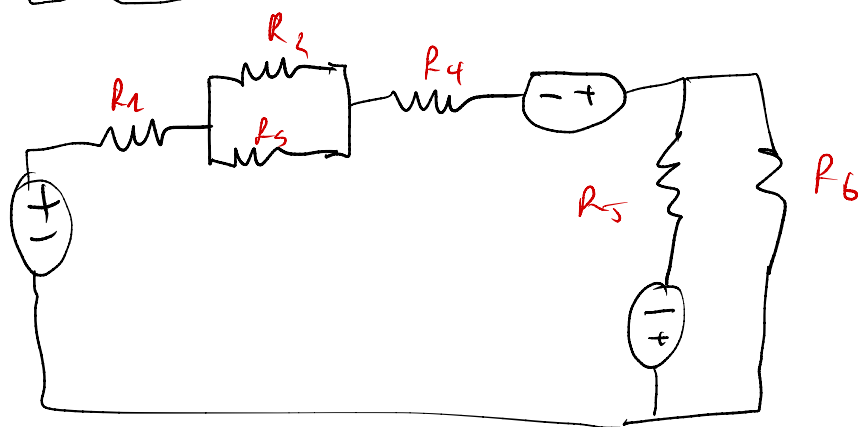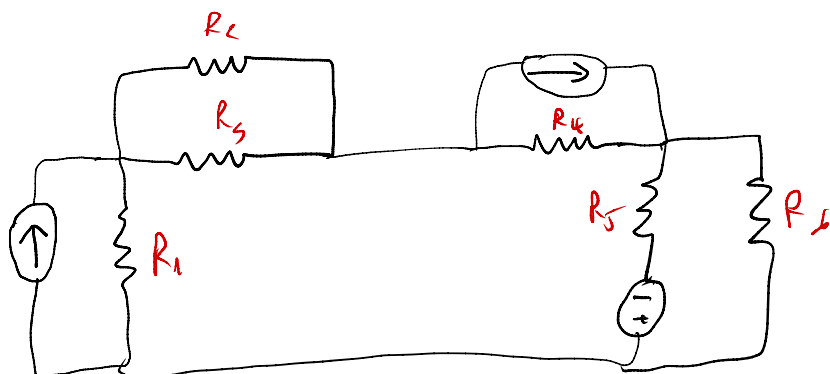
$$\rightarrow \text{Delivered power } P_{4A} = 40W$$



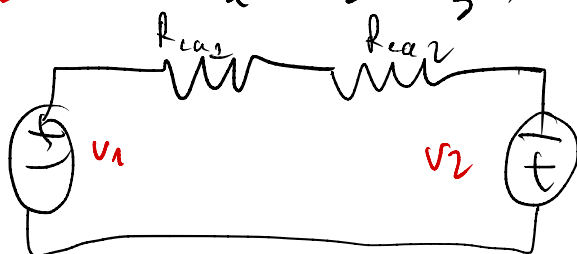
$$R_{eq} = R_1 + R_4 + (R_2 \parallel R_3)$$



$$(R_5 \parallel R_6)$$

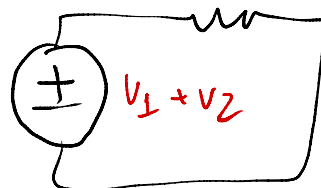

### Problem 3

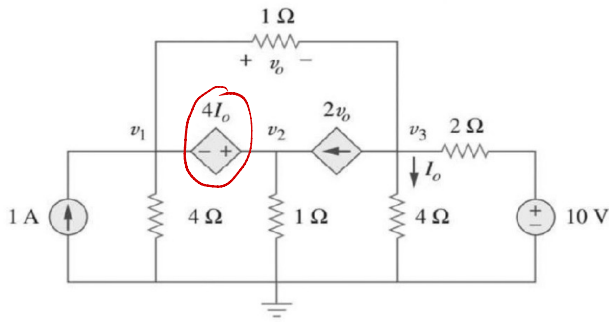

$$v_0 = v_1 - v_3 \quad 1I_0 = \frac{v_3}{4} \Rightarrow v_3 = v_2 - v_1$$

$$(1)(2) \quad v_1 - v_3 + \frac{v_1}{4} + v_2 - 2(v_1 - v_3) - 1 = 0$$

$$(3) \quad v_3 - v_1 + 2(v_1 - v_3) + \frac{v_3}{4} + \frac{v_3 - 10}{2} = 0$$

$$\Rightarrow \begin{cases} v_1 = \frac{164}{33} \\ v_2 = \frac{160}{33} \\ v_3 = -\frac{4}{33} \end{cases}$$

