

Name:

ID :

PRINCIPLES OF EE1

Homework #4

IMPORTANT: You should write on **A4 paper** that contains a full and detailed description of all the work done on the homework. Then you must submit the test hand-written by scanning and uploading the file in **pdf** form on Blackboard (Assignment Session). Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day).

Tip: You draw a bounding box or highlight for your final answer. Ex: $Y = ABC + AC = \boxed{ABC}$

Problem 1: (25 marks) Perform some operations below.

In rectangular form:

- a. $(4.2 + j6.8) + (7.6 + j0.2)$
- b. $(4 \times 10^{-6} + j76) + (7.2 \times 10^{-7} - j5)$
- c. $42\angle 45^\circ + 62\angle 60^\circ - 70\angle 120^\circ$

In polar form:

- d. $(400 - j200)(-0.01 - j0.5)(-1 + j3)$
- e. $\frac{-4.5 - j6}{0.1 - j0.8}$
- f. $\frac{42\angle 10^\circ}{7\angle 60^\circ}$
- g. $\frac{8\angle 60^\circ}{(2\angle 0^\circ) + (100 + j400)}$
- h. $\frac{(6\angle 20^\circ)(120\angle -40^\circ)(3 + j8)}{(2\angle -30^\circ)}$

Solution:

- a. $11.8 + j7.0$
- b. $4.72 \times 10^{-6} + j71$
- c. $(29.698 + j29.698) + (31.0 + j53.69) - (-35 + j60.62) = 95.7 + j22.77$
- d. $707.2 \angle -9.27^\circ$
- e. $9.30 \angle -43.99^\circ$
- f. $6.0 \angle -50^\circ$

g. $19.38 \times 10^{-3} \angle -15.69^\circ$ ✓

h. $3.07 \times 10^3 \angle 79.44^\circ$

Problem 2: (25 marks)

The maximum amplitude of a sinusoidal current is 40A . The current passes through one complete cycle in 0.5 ms . The magnitude of the initial current is 10 A . Finding the characteristics of a Sinusoidal Current via questions as below:

a. What is the frequency (in Hz) of the current?

b. What is the frequency in rad/s?

c. Write the expression for $i(t)$ using the cosine function. Express ϕ in degrees.

d. What is the rms value of the current?

Solution:

a. We have: $T = 0.5\text{ ms}$. So

b. $\omega = 2\pi f = 4000\pi\text{ rad/s}$.

c.

We have:

$$i(t) = I_m \cos(\omega t + \phi) = 40 \cos(2000\pi t + \phi),$$

and $i(0) = 10\text{ A}$.

$$\Rightarrow 10 = 40 \cos \phi \Rightarrow$$

$$\phi = 75.5^\circ$$

Thus, the expression for $i(t)$:

$$i(t) = 40 \cos(4000\pi t + 75.5^\circ).$$

d.

From $I_{rms} = \frac{I_m}{\sqrt{2}}$, we get the rms value of a sinusoidal current is $40/\sqrt{2}$.

Therefore, the rms value is:

$$I_{rms} = \frac{40}{\sqrt{2}} = 28.28\text{ A}.$$

Problem 3: (25 marks)

Determine the total input impedance Z_{in} of the following circuit

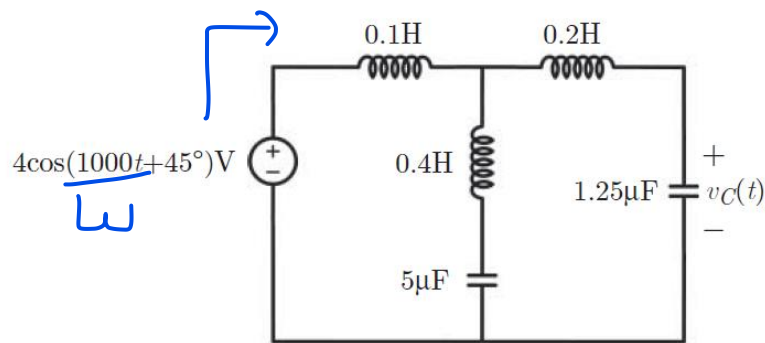



Figure 1

Solution:

We have: $\omega = 1000 \frac{\text{rad}}{\text{s}}$

The impedances of some circuit elements are calculated:

$$\begin{aligned}
 & \left\{ \begin{array}{l} 0.1 \text{ H} \longrightarrow j \times 1000 \times 0.1 = j100 \Omega, \\ 0.2 \text{ H} \longrightarrow j \times 1000 \times 0.2 = j200 \Omega, \\ 0.4 \text{ H} \longrightarrow j \times 1000 \times 0.4 = j400 \Omega, \end{array} \right. \quad j\omega L \\
 & \left\{ \begin{array}{l} 1.25 \mu\text{F} \longrightarrow 1 / (j \times 1000 \times 1.25 \times 10^{-6}) = -j800 \Omega, \\ 5 \mu\text{F} \longrightarrow 1 / (j \times 1000 \times 5 \times 10^{-6}) = -j200 \Omega \end{array} \right. \quad \frac{1}{j\omega C}
 \end{aligned}$$

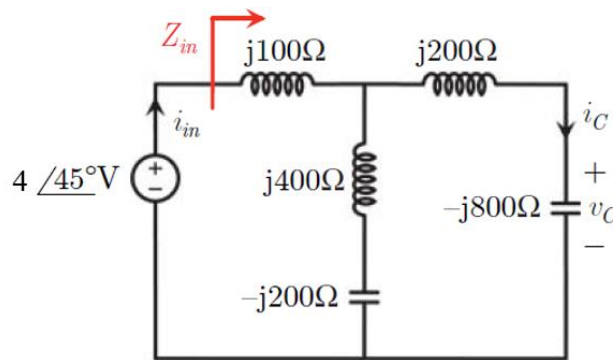

The total impedance:

$$\begin{aligned}
 Z_{in} &= j100 + [(j400 - j200) \parallel (j200 - j800)] \\
 &= j100 + \frac{j200 \times (-j600)}{j200 - j600} = j100 + j300 = \mathbf{j400 \Omega}.
 \end{aligned}$$

Problem 4: (25 marks)

✓

In the following circuit, the voltage source is $v_s(t) = 3\sqrt{2} \cos(2000t + 45^\circ)V$

a/ Find $v_L(t)$ in steady state.

b/ Compare phase angle between $v_L(t)$ and voltage source, state which one is leading?

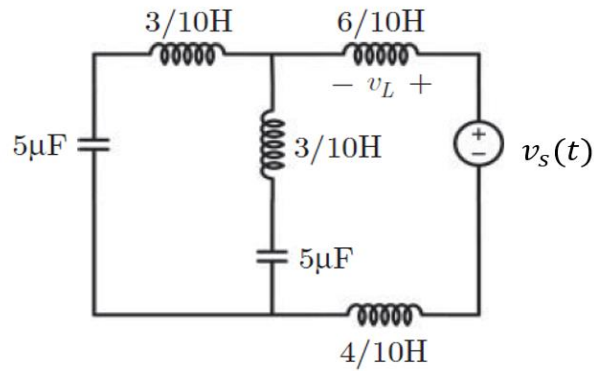


Figure 2

Solution:

a/

ω ✓ =


We have: $v_s(t) = 3\sqrt{2} \cos(2000t + 45^\circ)V \rightarrow 3\sqrt{2} \angle 45^\circ = 3(1 + j)V$,

The impedances of some circuit elements are calculated:

- $\mathcal{L} \left\{ \begin{array}{l} \bullet 3/10H \rightarrow j \times 2000 \times 3/10 = j600\Omega, \\ \bullet 4/10H \rightarrow j \times 2000 \times 4/10 = j800\Omega, \\ \bullet 6/10H \rightarrow j \times 2000 \times 6/10 = j1200\Omega, \end{array} \right.$
- $\mathcal{C} \left\{ \bullet 5\mu F \rightarrow 1/(j \times 2000 \times 5 \times 10^{-6}) = -j100\Omega, \right.$

jωL

$\frac{1}{j\omega C}$

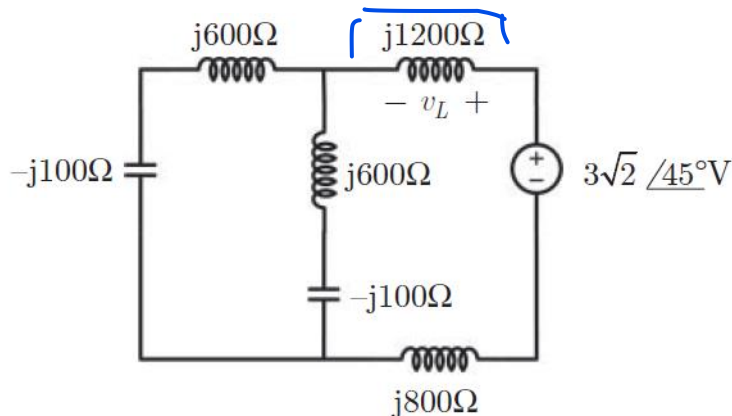

The total impedance:

$$\underline{Z_{in}} = (j600 - j100) \parallel (j600 - j100) + j1200 + j800 = j2250 \Omega.$$

The current through inductor $j1200$: $\underline{I_L} = \frac{3+j3}{j2250} = \frac{1+j}{750} (A)$

The voltage through inductor $j1200$: $\underline{V_L} = j1200 \times \underline{I_L} = \frac{8+j8}{5} = \frac{8\sqrt{2}}{5} \angle 45^\circ (A)$

So, in time domain: $\underline{v_L(t) = 2.26\cos(2000t + 45^\circ)}$

b/

The voltage of the inductor $v_L(t)$ is in phase with the voltage source.