

PRINCIPLES OF EE1

HW

Deadline: 8:00, 1 JUNE 2024

INSTRUCTIONS: Students scan and upload answer into Blackboard

Question 1:

Find the rms value of the half-wave rectified sinusoidal voltage shown in Fig1

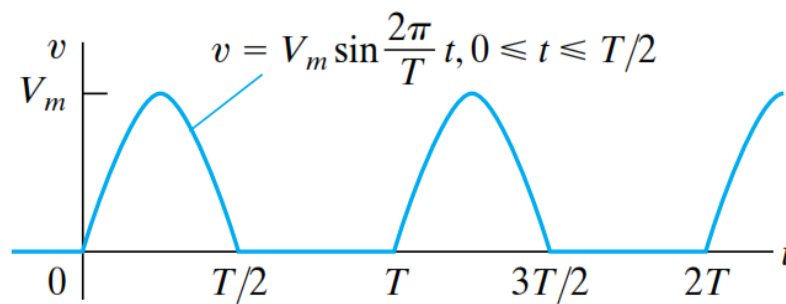


Fig.1

Question 2:


Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric expression:

- a) $y = 30 \cos(200t - 160^\circ) + 15 \cos(200t + 70^\circ)$,
- b) $y = 90 \sin(50t - 20^\circ) + 60 \cos(200t - 70^\circ)$,

Question 3:

A 400 Hz sinusoidal voltage with a maximum amplitude of 100 V is applied across the terminals of an inductor. The maximum amplitude of the steady-state current in the inductor is 20 A.


- a) What is the frequency of the inductor current?
- b) If the phase angle of the voltage is zero, what is the phase angle of the current?
- c) What is the inductive reactance of the inductor?
- d) What is the inductance of the inductor in millihenrys?
- e) What is the impedance of the inductor?

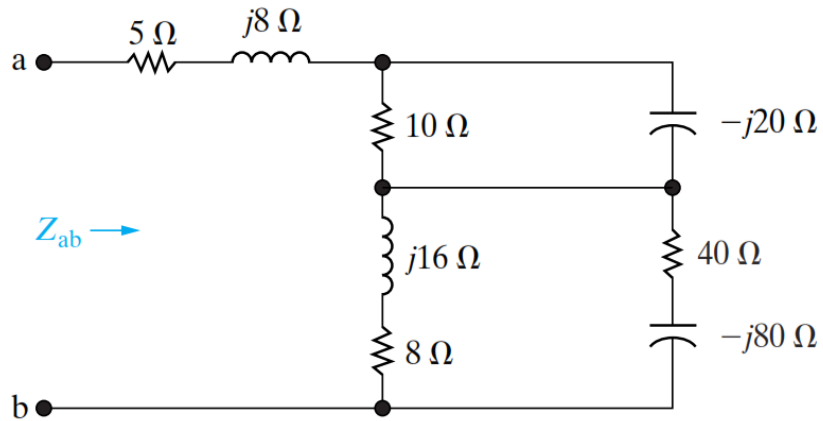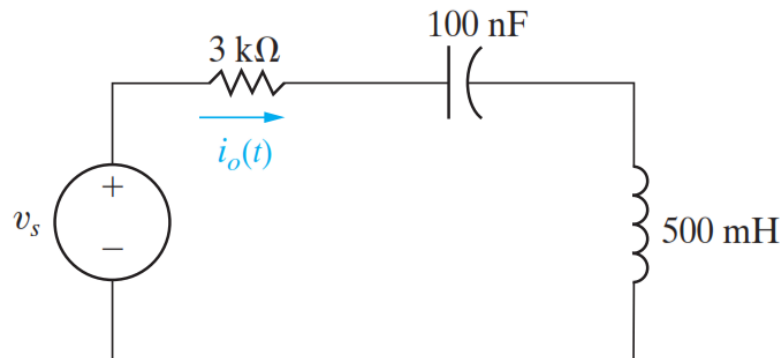Question 4:

Find the impedance Z_{ab} in the circuit in both polar and rectangular form

Question 5:

Find the steady-state expression $i_o(t)$ for in the circuit , $v_s = 80 \cos(2000t)$ V

**Question 6:**

Find the steady-state expression $v_o(t)$ for in the circuit , $v_g = 60 \sin(8000t)$ V

