



International University  
School of Electrical Engineering

## PRINCIPLES OF ELECTRICAL ENGINEERING 2

Lecture # 8b Supplement

# FREQUENCY RESPONSE OF AC CIRCUIT

- Some Preliminaries

- ✓ Analysis of a circuit with varying frequency of a sinusoidal sources is called the **frequency response** of a circuit.
- ✓ Frequency selection in the circuits are called filters because of their ability to filter out certain input signals on the basis of frequency.



# TRANSFER FUNCTION (TF or tf)


- Frequency response can be obtained by using transfer function.



- DEFINITION: Transfer function,  $H(\omega)$  is a ratio between output & input signals (in  $s$ -domain or  $j\omega$ ).

$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

# TRANSFER FUNCTION

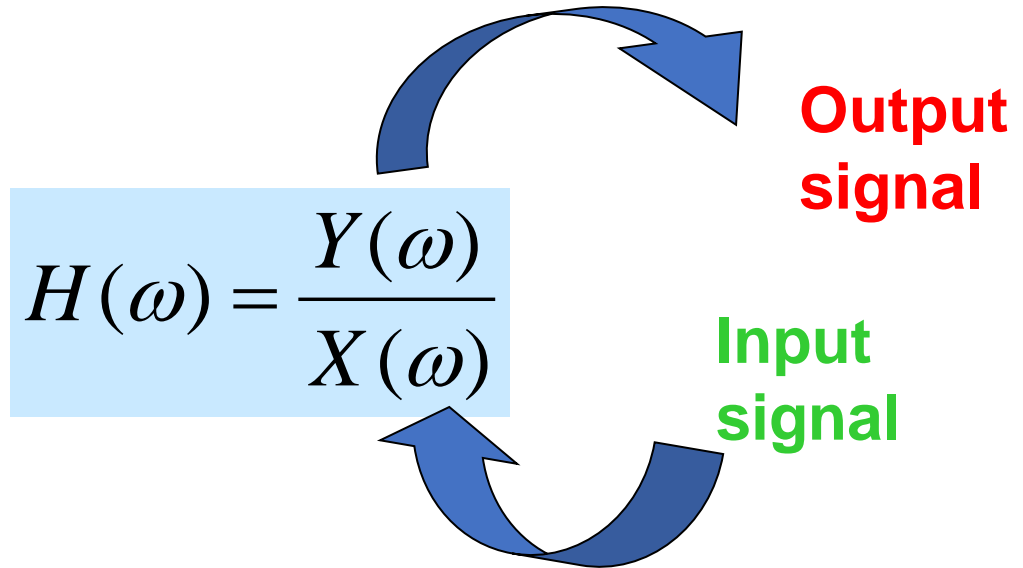

$$H(\omega) = |H(\omega)| \angle \phi = H e^{j\phi}$$

Using sinusoidal source, the transfer function will be the **magnitude** and **phase** of output voltage to the magnitude and phase of input voltage of a circuit .

## 4 conditions of TF:

$$H(\omega) = \text{voltage gain} = \frac{V_o(\omega)}{V_i(\omega)}$$

$$H(\omega) = \text{current gain} = \frac{I_o(\omega)}{I_i(\omega)}$$

$$H(\omega) = \text{impedance} = \frac{V(\omega)}{I(\omega)}$$

$$H(\omega) = \text{admittance} = \frac{I(\omega)}{V(\omega)}$$

**Because there is no unit, they are called GAIN**

# POLES & ZEROS


- Transfer function is written in fraction
- The numerator and denominator can be existed as a polynomial

$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$



$$H(\omega) = \frac{N(\omega)}{D(\omega)}$$

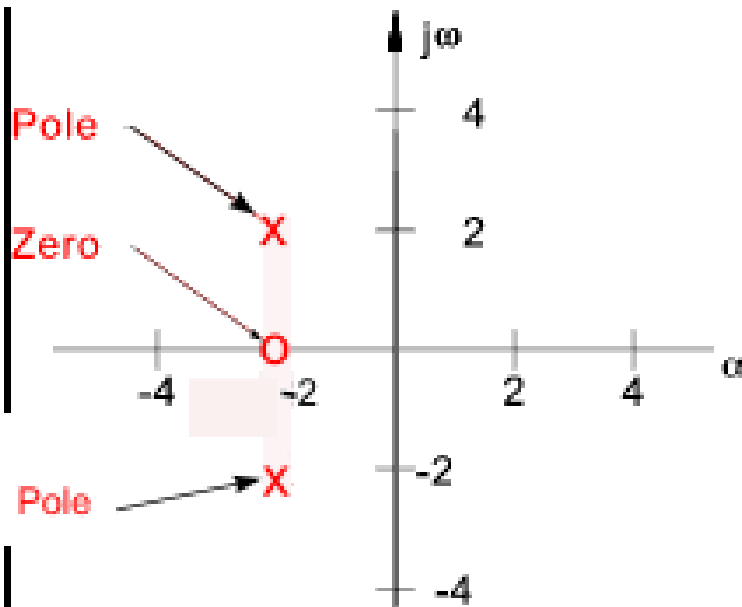- The roots of numerator also known as **ZEROS**. Zeros exist when  $N(\omega)=0$
- The roots of denominator also known as **POLES**. Poles exist when  $D(\omega)=0$



- The symbol for pole is **x**
- The symbol for zero is **o**
- Complex s-plane is used to plot poles and zeros.

# POLES/ZEROS


Poles/zeros  
at the origin




real zero




quadratic zero

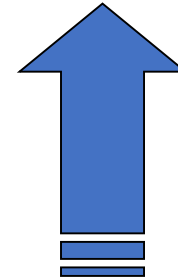
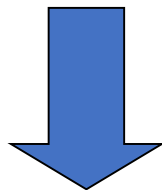
$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega / z_1) [1 + j2\xi_1\omega / \omega_k + (j\omega / \omega_k)^2] \dots}{(1 + j\omega / p_1) [1 + j2\xi_2\omega / \omega_n + (j\omega / \omega_n)^2] \dots}$$



real pole

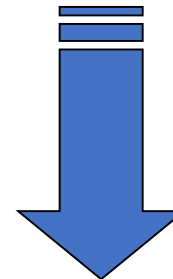

quadratic pole

# LOCATION OF POLES/ZEROS

- Zeros/poles at the origin: Zeros/poles that are located at 0
- Real Zeros/poles: Zeros/poles that are located at real axis (-1, -2, 1, 2, 10, etc.)
- Quadratic Zeros/poles: Zeros/poles that are not located at imaginary or real axis (-1+j2, 2+j5, 3-j3, etc.)

## EXAMPLE

$$H(\omega) = \frac{j\omega(j\omega+1)(j\omega+2)}{(j\omega+1)(j\omega+4)}$$

Simplified,

$$H(\omega) = \frac{j\omega(j\omega+2)}{(j\omega+4)}$$




Simplified,

$$H(\omega) = \frac{j\omega(j\omega + 2)}{(j\omega + 4)}$$

## ZEROS


- Let numerator,  $N(\omega)=0$

$$j\omega(j\omega + 2) = 0$$

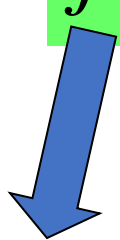

1st zero:

$$j\omega = 0$$

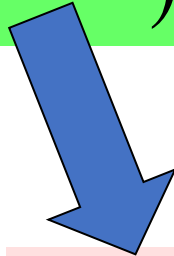

2nd zero:

$$j\omega + 2 = 0$$

$$\therefore j\omega = -2$$

## POLE

- Let denominator,  $D(\omega)=0$

$$(j\omega + 4) = 0$$



pole:

$$j\omega + 4 = 0$$


$$\therefore j\omega = -4$$

# Example

Find the input impedance  $Z_i(\omega)$ , poles and zeroes,  $\omega_n$  and  $\zeta$ .

$$Z_i(s) = \frac{V_o(s)}{I_o(s)} = \left( 5 + \frac{1}{s/10} \right) \parallel (3 + 2s)$$
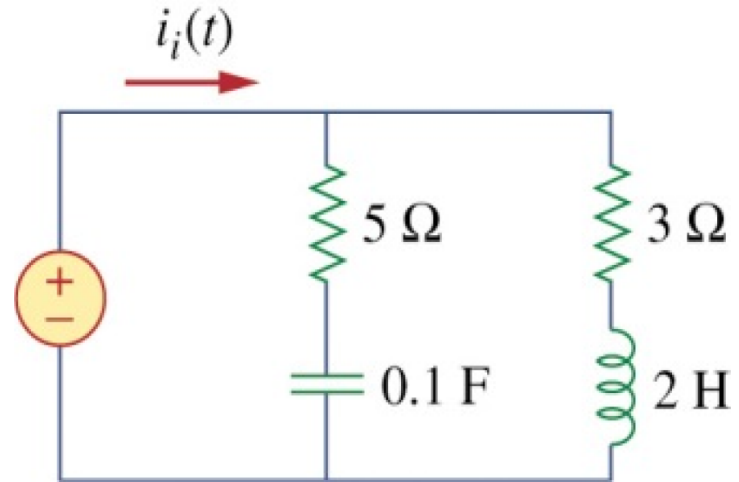
$$Z_i(s) = \frac{(5 + 10/s)(3 + 2s)}{5 + 10/s + 3 + 2s} = \frac{5(s + 2)(s + 1.5)}{s^2 + 4s + 5}$$



$$Z_i(\omega) = \frac{5(j\omega + 2)(j\omega + 1.5)}{(j\omega)^2 + 4j\omega + 5} = 3 \frac{\left(1 + j\frac{\omega}{2}\right)\left(1 + j\frac{\omega}{1.5}\right)}{1 + j2\left(\frac{2}{\sqrt{5}}\right)\left(\frac{\omega}{\sqrt{5}}\right) + \left(j\frac{\omega}{\sqrt{5}}\right)^2} = K \frac{\left(1 + j\frac{\omega}{z_1}\right)\left(1 + j\frac{\omega}{z_2}\right)}{1 + j2\zeta\frac{\omega}{\omega_n} + \left(j\frac{\omega}{\omega_n}\right)^2}$$


$K = 3$ ,  $z_1 = 2$ ,  $z_2 = 1.5$ . Quadratic Pole: damping factor  $\zeta = \frac{2}{\sqrt{5}}$ ,  $\omega_n = \sqrt{5}$

zeros at  $s = j\omega = -2$  and  $-1.5$


Note that,  $z_1$  and  $z_2$  in this example are based on the transfer function definition mentioned before.

# FREQUENCY RESPONSE PLOT

- USING SEMILOG GRAPH

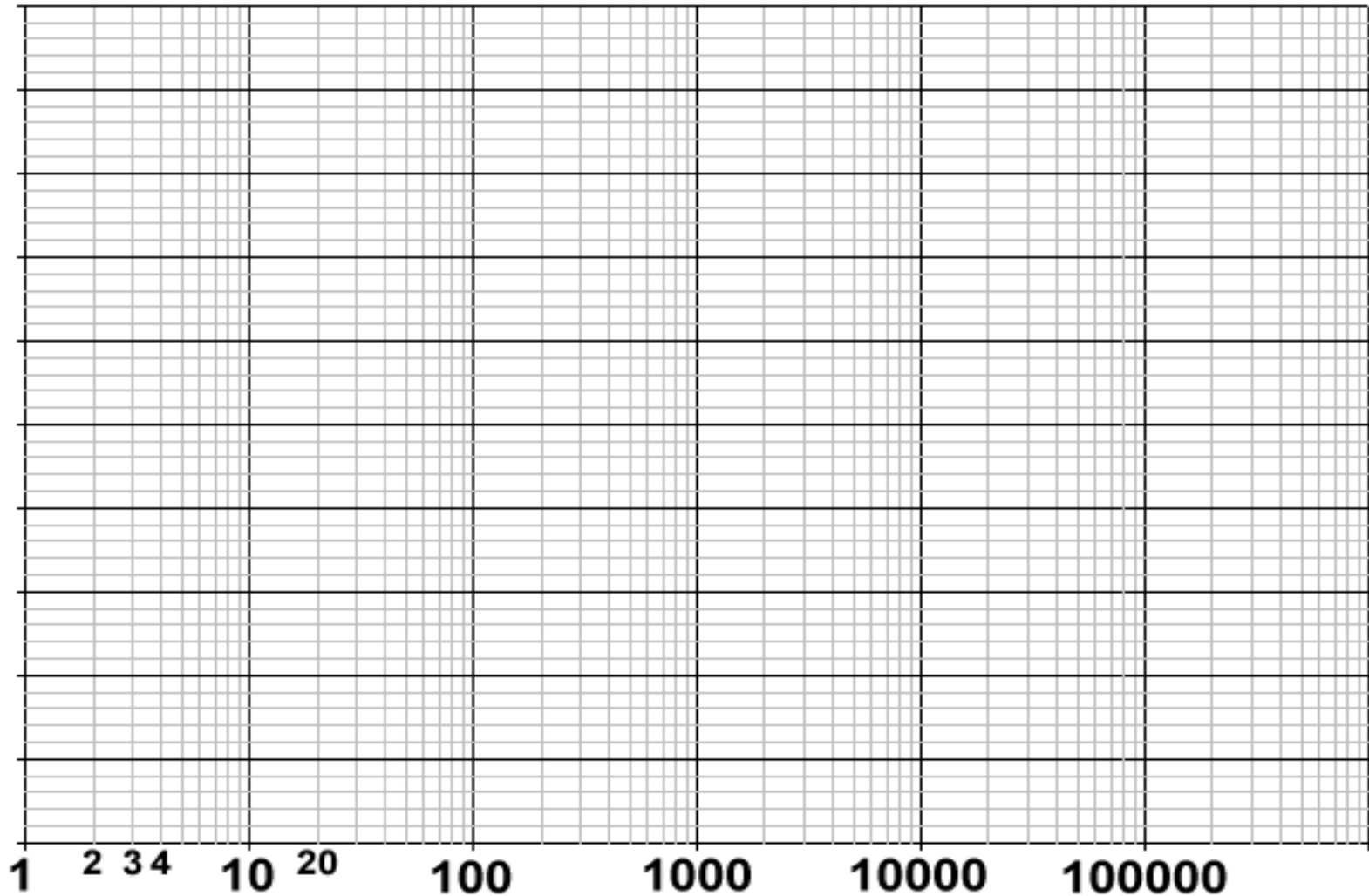

# Sketching a Log Frequency Scale

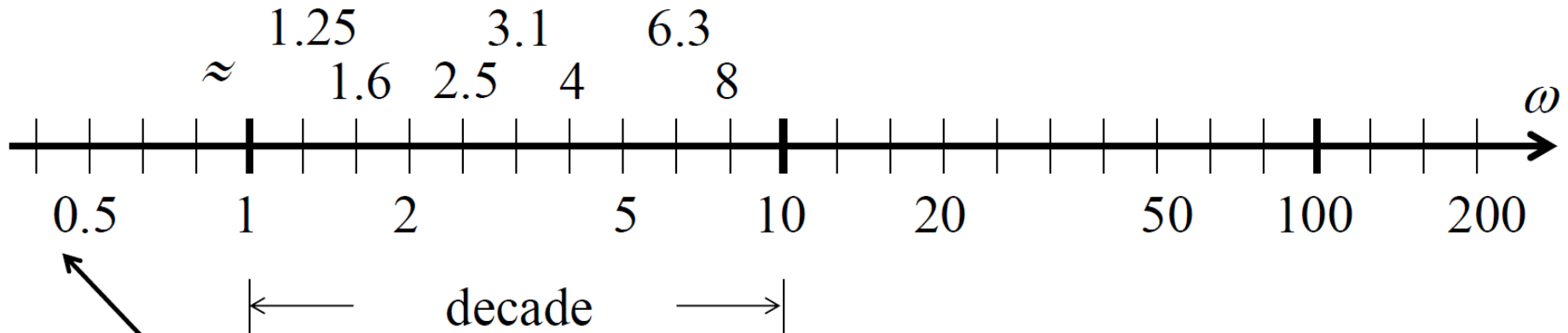

Note: There is no point  $\omega=0$  on a logarithmic frequency scale !


A decade is an interval between two frequencies with a ratio of 10; e.g., between  $\omega_0$  and  $10\omega_0$ , or between 10 Hz and 100 Hz.

# MAGNITUDE PLOT & PHASE PLOT

Using transfer function of circuit, we plot a frequency response of the circuit for both **amplitude** & **phase** with changing **source frequency**


- Magnitude plot

$|H(j\omega)|$  vs frequency( $\omega$ )

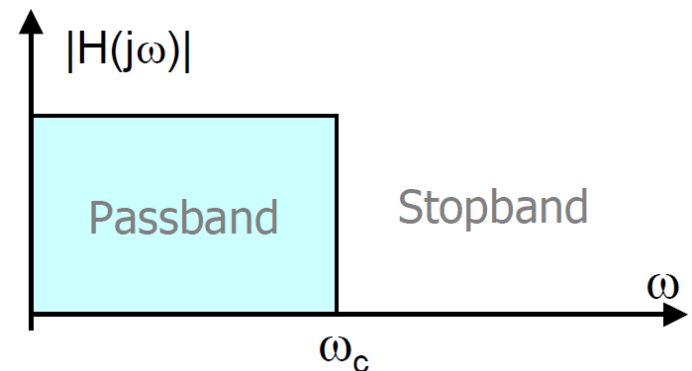


- Phase angle plot

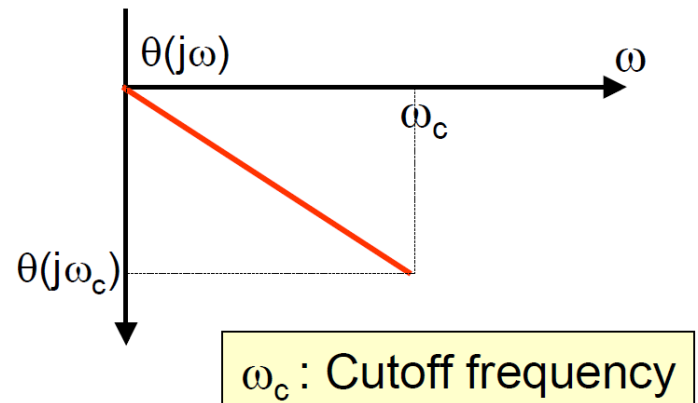$\theta(j\omega)$  vs frequency( $\omega$ )




# HOW TO DO MAGNITUDE AND PHASE PLOT

- i. Transform the time domain circuit (t) into freq. domain circuit ( $\omega$ )
- ii. Determine the TF,  $H(\omega)$
- iii. Plot the magnitude of that TF,  $|H(\omega)|$  against  $\omega$ .
- iv. Plot the phase of that TF,  $\phi(^{\circ})$  against  $\omega$ .

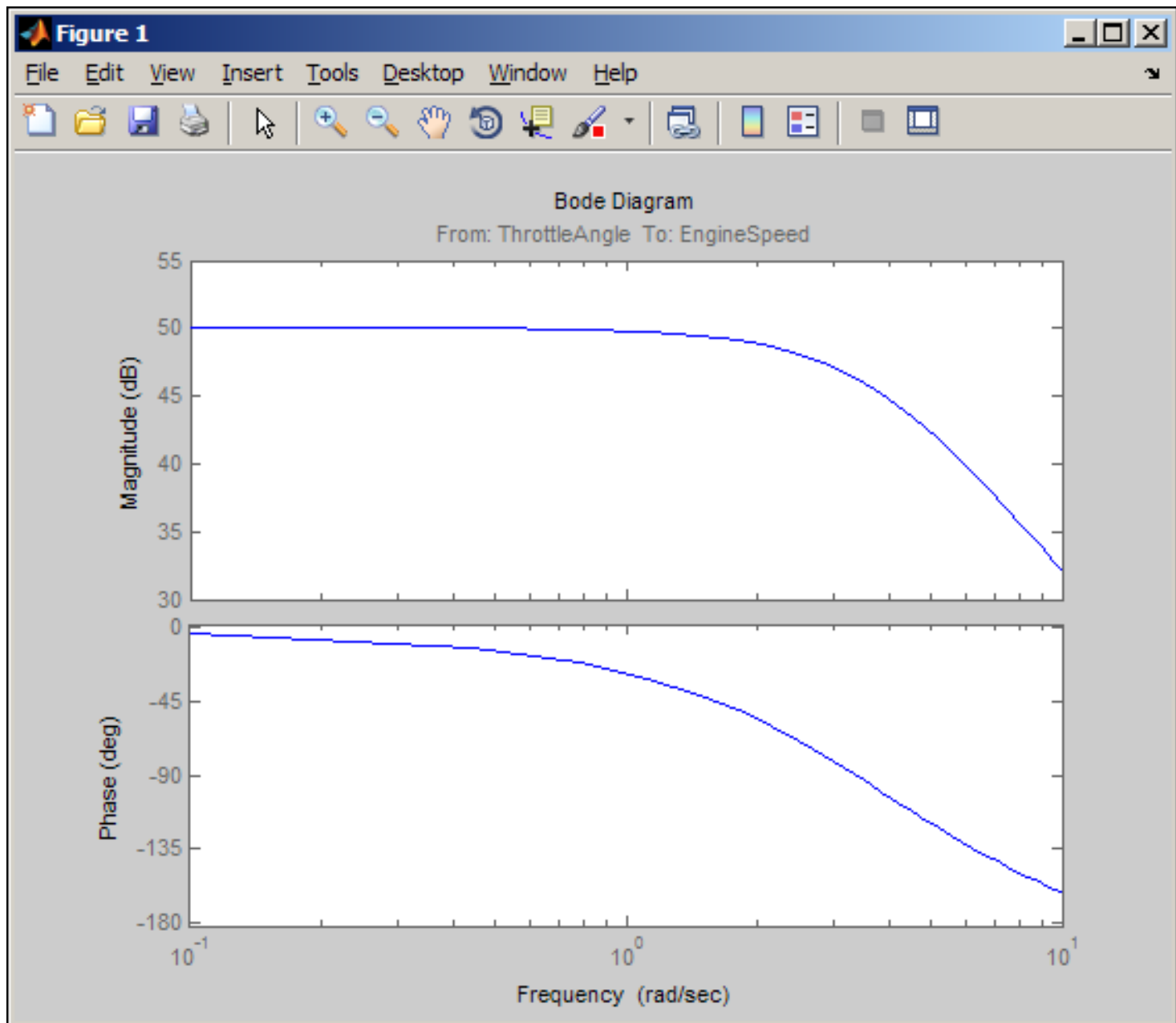


# THE CONCEPT OF TF

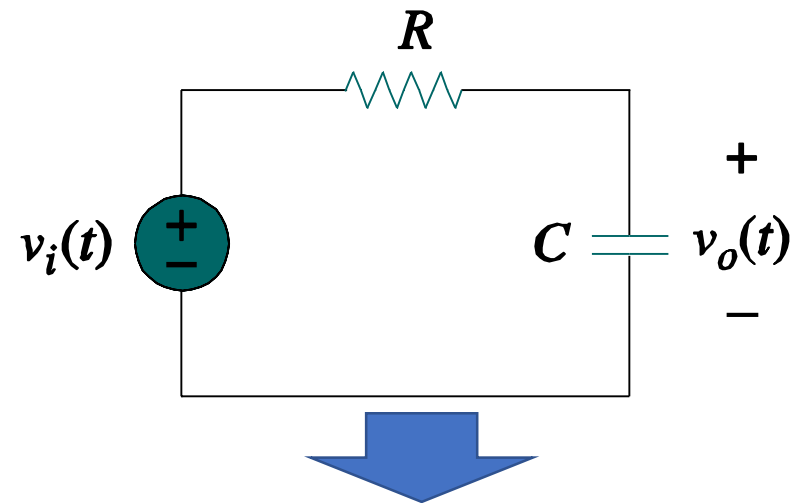

## CIRCUIT IN FREQUENCY DOMAIN

- Input is  $V_i$  & Output is  $V_o$ ,

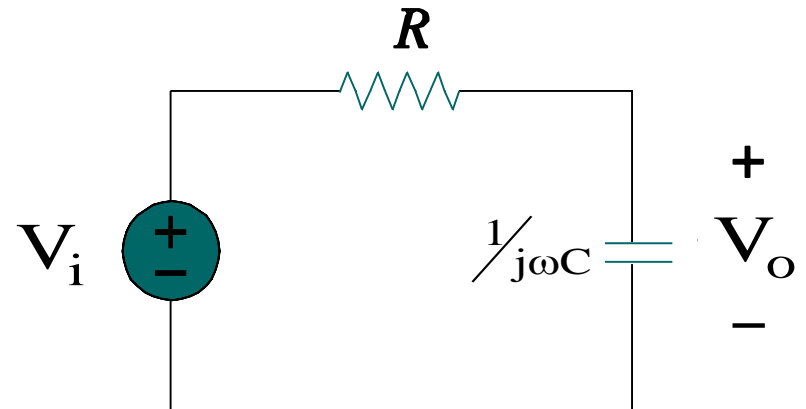

➔ OBTAINED THE TF:

$$\begin{aligned} H(\omega) &= \frac{V_o}{V_i} = \frac{1/j\omega C}{R + 1/j\omega C} \\ &= \frac{1}{1 + j\omega RC} \end{aligned}$$



## MAGNITUDE OF TF

$$H(\omega) = \frac{1}{1 + j\omega RC}$$



Magnitude;

$$\therefore |H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

If  $\omega_c = 1/RC$

$$\therefore |H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

## PHASE OF TF

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\phi = -\tan^{-1}\left(\frac{\omega RC}{1}\right) = -\tan^{-1}(\omega RC)$$

$$\text{If } \omega_c = 1/RC$$



$$\therefore \phi = -\tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$


## CUT-OFF FREQUENCY:

$$\omega_c = \frac{1}{RC}$$

# THE VALUES OF MAGNITUDE AND PHASE


$\omega/\omega_c$	$H$	$\phi$
0	1	0
1	0.71	$-45^\circ$
2	0.45	$-63^\circ$
3	0.32	$-72^\circ$
10	0.1	$-84^\circ$
20	0.05	$-87^\circ$
100	0.01	$-89^\circ$
$\infty$	0	$-90^\circ$

# MAGNITUDE PLOT

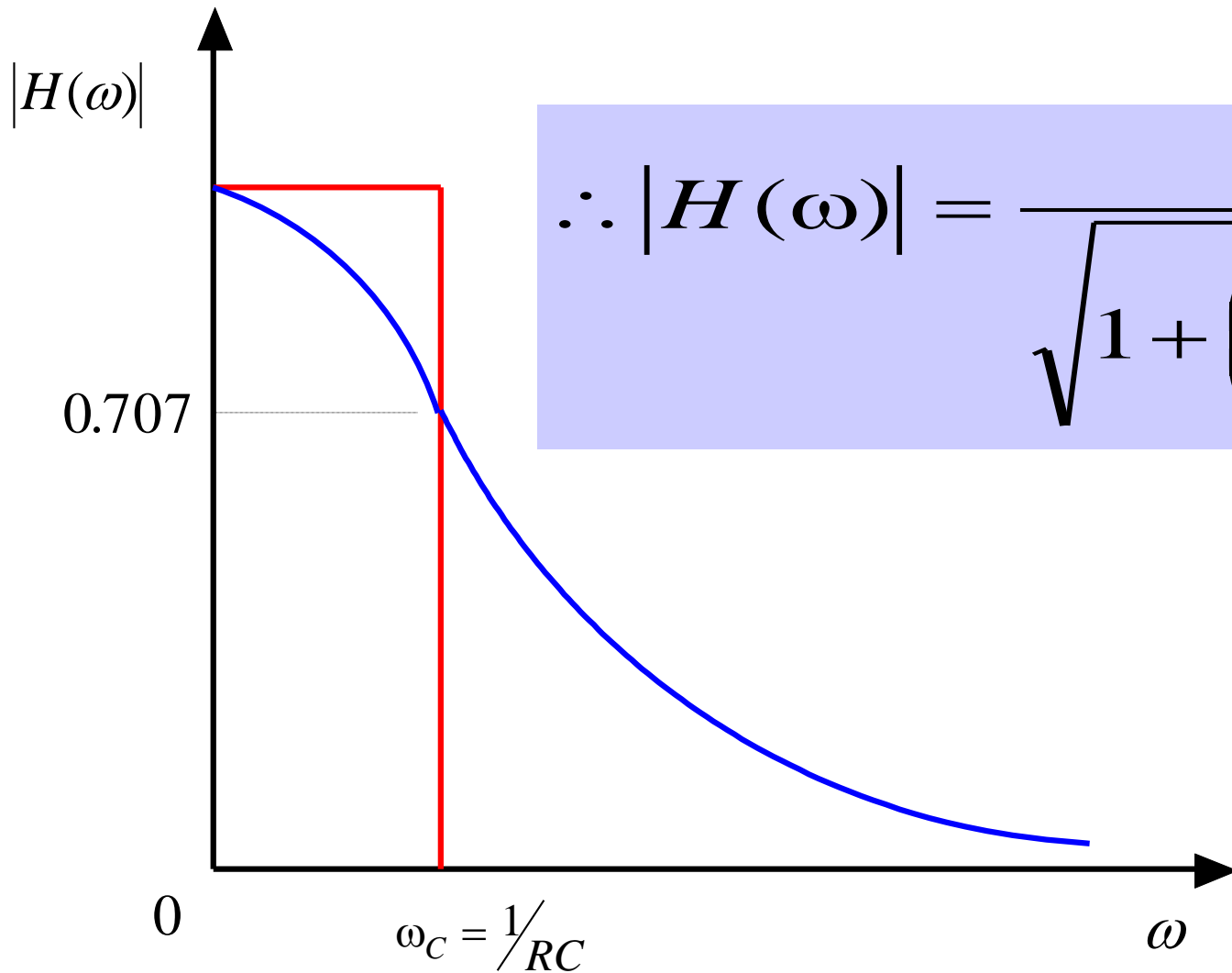

$$\therefore |H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

# PHASE PLOT

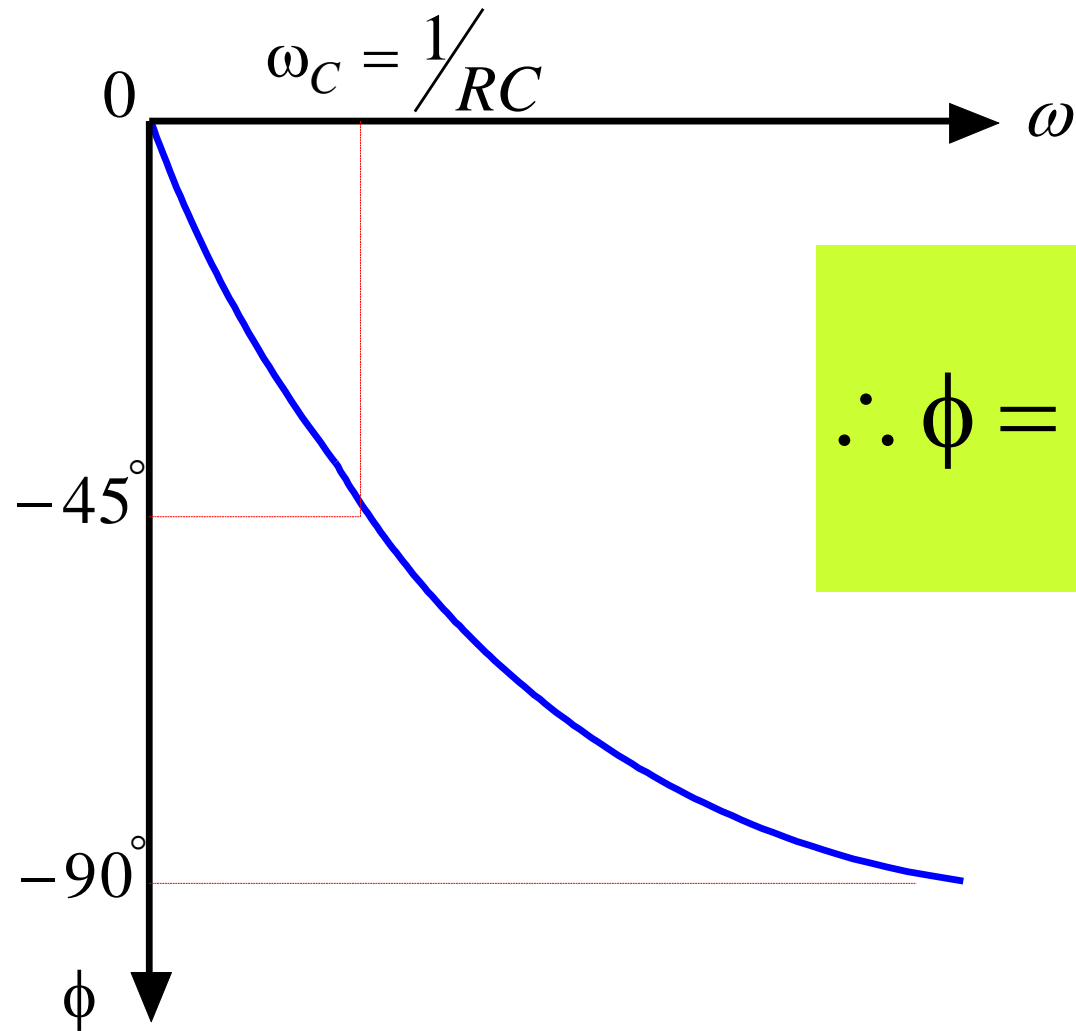

$$\therefore \phi = -\tan^{-1}\left(\frac{\omega}{\omega_C}\right)$$

# FREQUENCY RESPONSE PLOT

## BODE PLOTS

### Hendrik Wade Bode

From Wikipedia, the free encyclopedia

**Hendrik Wade Bode** (/ˈboʊdi/ *boh-dee*; Dutch: [ˈbɔdə]<sup>[1]</sup> (December 24, 1905 – June 21, 1982)<sup>[1]</sup> was an American engineer, researcher, inventor, author and scientist, of Dutch ancestry. As a pioneer of modern [control theory](#) and [electronic telecommunications](#) he revolutionized both the content and methodology of his chosen fields of research.

He made important contributions to the design, guidance and control of anti-aircraft systems during World War II and, continuing post-World War II during the [Cold War](#), to the design and control of missiles and [anti-ballistic missiles](#).<sup>[2]</sup>

He also made important contributions to [control system theory](#) and mathematical tools for the analysis of stability of [linear systems](#), inventing [Bode plots](#), [gain margin](#) and [phase margin](#).

Bode was one of the great engineering philosophers of his era.<sup>[3]</sup> Long respected in academic circles worldwide,<sup>[4]</sup><sup>[5]</sup> he is also widely known to modern engineering students mainly for developing the [asymptotic](#) magnitude and [phase](#) plot that bears his name, the [Bode plot](#).

His research contributions in particular were not only multidimensional but far

**Hendrik Wade Bode**



Hendrik Wade Bode

<b>Born</b>	December 24, 1905 <a href="#">Madison, Wisconsin</a>
<b>Died</b>	June 21, 1982 (aged 76) <a href="#">Cambridge, Massachusetts</a>
<b>Residence</b>	<a href="#">Cambridge, Massachusetts</a>
<b>Nationality</b>	American

# FREQUENCY RESPONSE PLOT

## BODE PLOTS

Bode plots are semilog plots of **magnitude (in decibels)** and **phase (in degrees)** of a transfer function versus **frequency**

### DECIBEL SCALE

### Logarithm

$$\log P_1 P_2 = \log P_1 + \log P_2$$

$$\log P_1 / P_2 = \log P_1 - \log P_2$$

$$\log P^n = n \log P$$

$$\log 1 = 0$$

# BODE PLOT CHARACTERISTIC FOR POLES & ZEROS

Logarithm of TF:

$$H(\omega) = \frac{N(\omega)}{D(\omega)}$$
$$\therefore \log H = \log[N] - \log[D]$$

Generally, the power gain is measured in *bels*

$$G = \text{Number of } \textit{bels} = \log_{10} \frac{P_2}{P_1}; \text{ (} P_1 \text{ and } P_2 \text{ are power.)}$$

- Decibel (dB) is 1/10<sup>th</sup> of a *bel*, and is

$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1}$$

$$G_{dB} = 20 \log_{10} \frac{V_2}{V_1}$$



# TRANSFER FUNCTION

$$\mathbf{H} = H \angle \phi = H e^{j\phi}$$


$$H_{\text{dB}} = 20 \log_{10} H$$

Magnitude $H$	$20 \log_{10} H$ (dB)
0.001	-60
0.01	-40
0.1	-20
0.5	-6
$1/\sqrt{2}$	-3
1	0
$\sqrt{2}$	3
2	6
10	20
20	26
100	40
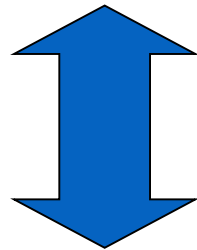
# GENERAL EQUATION/STANDARD FORM OF TF

- Before draw, make sure the general equation of tf is obtained first:

$$H(\omega) = \frac{K(j\omega)^{\pm} (1 + j\omega/z_1) [(j\omega)^2 + 2\xi_1\omega_n + \omega_n^2]}{(1 + j\omega/p_1) [(j\omega)^2 + 2\xi_2\omega_n + \omega_n^2]}$$



**COMPARE**

Ex.

$$H(\omega) = \frac{2(j\omega)(j\omega + 1) [(j\omega)^2 + 30\omega + 100]}{(j\omega + 2) [(j\omega)^2 + 50\omega + 400]}$$

$\xi$  is called the damping factor

$$H(\omega) = \frac{2(j\omega)(1 + j\omega/1)[(j\omega)^2 + 30\omega + 10^2]}{(1 + j\omega/2)[(j\omega)^2 + 50\omega + 20^2]}$$

Constant:

$$K = 2$$

Zero at the origin:

$$j\omega = 0$$

Real zero:

$$j\omega = 1$$

Quadratic zero:

$$\omega_n = 10$$

Real pole:

$$j\omega = 2$$

Quadratic pole:

$$\omega_n = 20$$

# Bode Plots


## Steps to construct a Bode plot

- Plot each factor **separately**.
  - **Additively combine all of them graphically** because of the **logarithms** involved
- 
- The mathematical convenience of the logarithm makes the Bode plots a powerful tool.
  - **Straight-line plots** used instead of actual plots

# BODE PLOT OF A CONSTANT, K

## (1) (GAIN)

constant

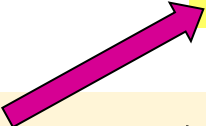
$$H(\omega) = \frac{K(j\omega)^{\pm} (1 + j\omega/z_1) [(j\omega)^2 + 2\xi_1\omega_n + \omega_n^2]}{(1 + j\omega/p_1) [(j\omega)^2 + 2\xi_2\omega_n + \omega_n^2]}$$

## CHARACTERISTICS

- Magnitude for constant is :  $H = 20\log|K|$
- Phase angle for constant is:  $\phi = 0^\circ$

# BODE PLOT FOR CONSTANT


$$\mathbf{H}^{\text{const}}(\omega) = K$$

$$\Rightarrow H_{\text{dB}}^{\text{const}} = 20 \log_{10} |K|$$


$$\Rightarrow \begin{cases} \phi = 0^\circ & \text{if } K > 0 \\ \phi = \pm 180^\circ & \text{if } K < 0 \end{cases}$$

For the gain  $K$ , the magnitude is  $20 \log_{10}(K)$  and the phase is  $0^\circ$ ; both are constant with frequency. If  $K$  is negative, the magnitude is  $20 \log_{10}(|K|)$  but the phase is  $\pm 180^\circ$ .

- magnitude plot

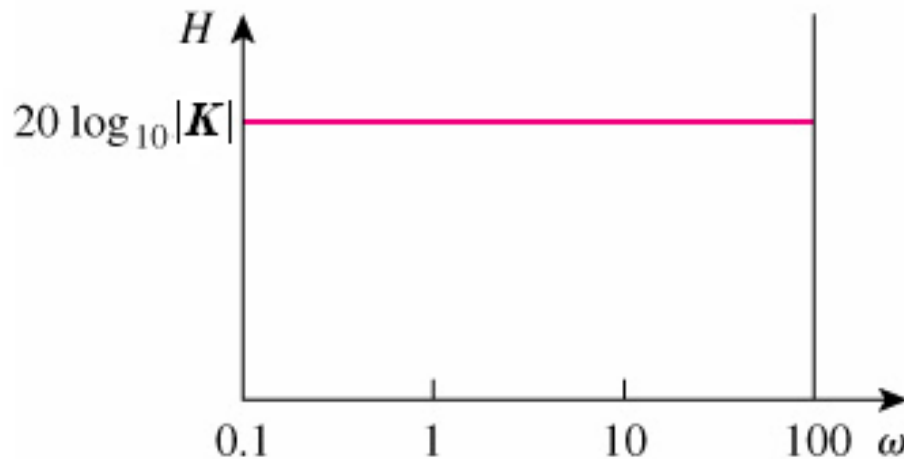

- phase plot

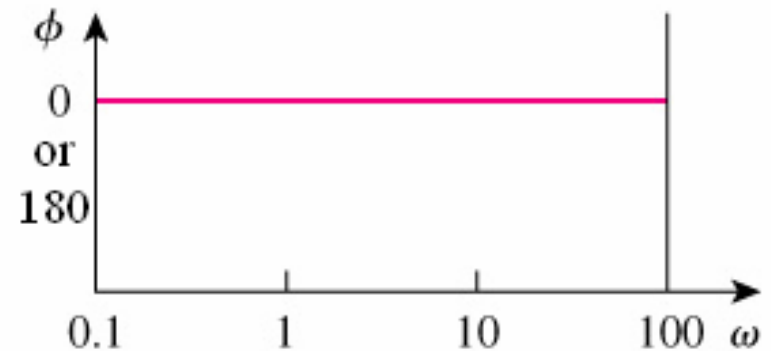

# BODE PLOT FOR ZERO AT THE ORIGIN

## (2) ZERO AT THE ORIGIN $(j\omega)^N$

$$H(\omega) = \frac{K(j\omega)^{\pm}(1 + j\omega/z_1)[(j\omega)^2 + 2\xi_1\omega_n + \omega_n^2]}{(1 + j\omega/p_1)[(j\omega)^2 + 2\xi_2\omega_n + \omega_n^2]}$$

$$\mathbf{H}^{\text{origin\_zero}}(\omega) = j\omega = \omega \angle 90^\circ$$

$$\Rightarrow \begin{cases} H_{\text{dB}}^{\text{origin\_zero}} = 20 \log_{10} \omega \\ \phi = 90^\circ \end{cases}$$


## (2) ZERO AT THE ORIGIN $(j\omega)^N$

For the zero  $(j\omega)$  at the origin, the magnitude is  $20 \log_{10}(\omega)$  and the phase is  $90^\circ$ .


The slope of the magnitude plot is 20 dB/decade, while the phase is  $90^\circ$  and constant with frequency.

The Bode plots for the pole  $1/(j\omega)$  are similar except that the slope of the magnitude plot is  $-20$  dB/decade while the phase is  $-90^\circ$ .

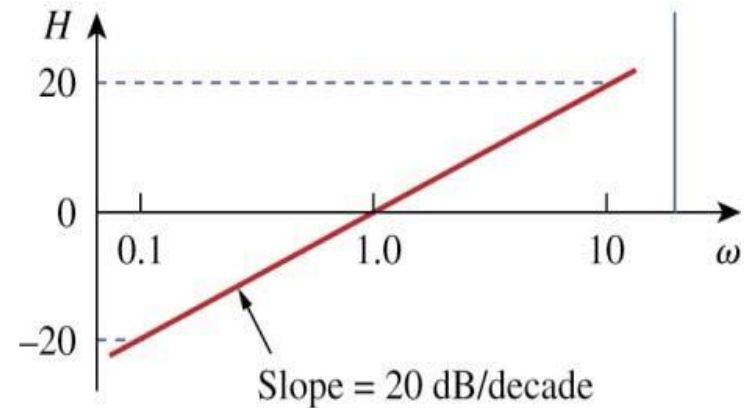In general, for  $(j\omega)^N$ , where  $N$  is an integer, the magnitude plot will have a slope of  $20N$  dB/decade, while the phase is  $90N$  degrees.



(a)

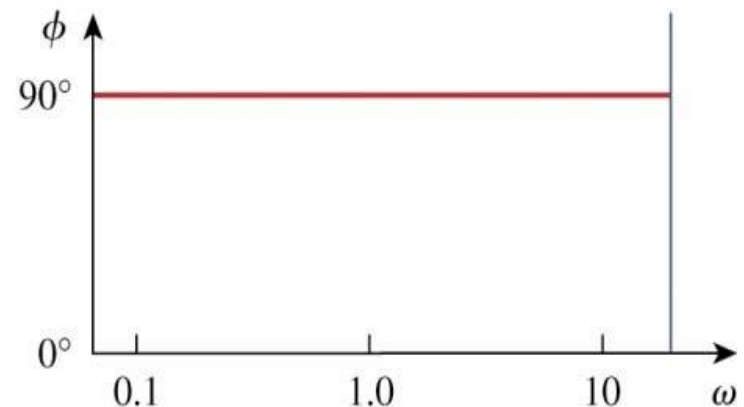

(b)



# CHARACTERISTIC OF $(j\omega)^N$

- **Magnitude:**

- Straight line with 20dB/decade of slope that has a value of 0 dB at  $\omega=1$



$$H = 20N \text{ (dB/dec)}$$

Thus,  $\pm 20$  dB/decade means that the magnitude changes  $\pm 20$  dB whenever the frequency changes tenfold or one decade.

- **Phase:**


$$\phi = 90N^\circ$$

## MAGNITUDE PLOT

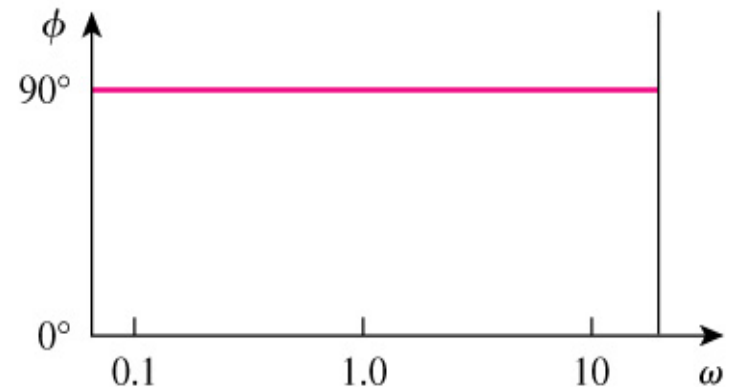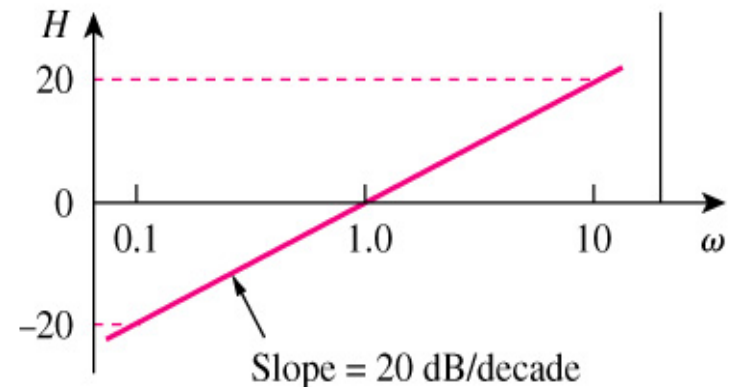

## PHASE PLOT

# CHARACTERISTIC OF $(j\omega)^N$

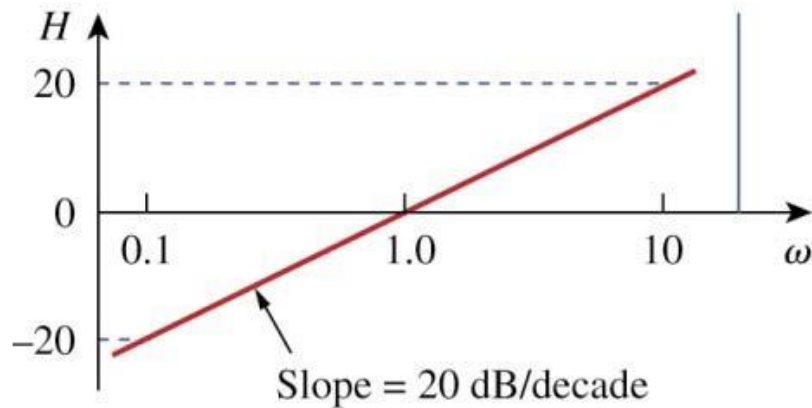

$$H(\omega) = K \cdot j\omega, \text{ slope} = +20 \text{ dB/decade}$$

$$K = ? \quad |H(\omega = 1)| = K$$

$$H_{dB} = 20 \log_{10}(K) = 0 \text{ dB} \Rightarrow K = 1$$

$$\text{If } H(\omega) = K \cdot (j\omega)^2, \text{ slope} = +40 \text{ dB/decade}$$

$$\text{If } H(\omega) = \frac{K}{j\omega} \Rightarrow \text{slope} = -20 \text{ dB/decade}$$

# BODE PLOT OF POLE AT THE ORIGIN

### (3) POLE AT THE ORIGIN $1/(j\omega)^N @ (j\omega)^{-N}$

$$H(\omega) = \frac{K(1 + j\omega/z_1) \left[ (j\omega)^2 + 2\xi_1\omega_n + \omega_n^2 \right]}{(j\omega)^{\pm} (1 + j\omega/p_1) [(j\omega)^2 + 2\xi_2\omega_n + \omega_n^2]}$$

$$\mathbf{H}^{\text{origin\_pole}}(\omega) = (j\omega)^{-1} = \omega^{-1} \angle -90^\circ$$
$$\Rightarrow \begin{cases} H_{\text{dB}}^{\text{origin\_pole}} = -20 \log_{10} \omega \\ \phi = -90^\circ \end{cases}$$



# CHARACTERISTIC OF $(j\omega)^{-N}$

- Magnitude:
  - Straight line with - 20dB/dec of slope that has a value of 0 dB at  $\omega=1$

$$H = -20N \text{ (dB/dec)}$$

- Phase:

$$\phi = -90N^\circ$$

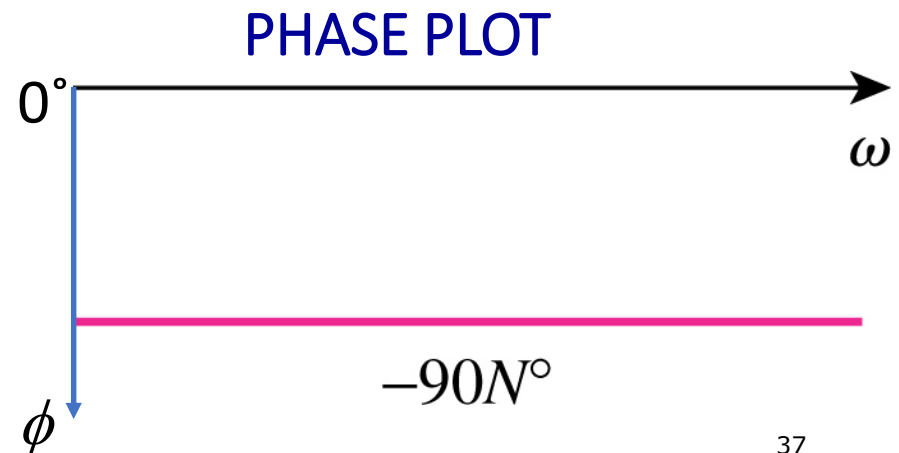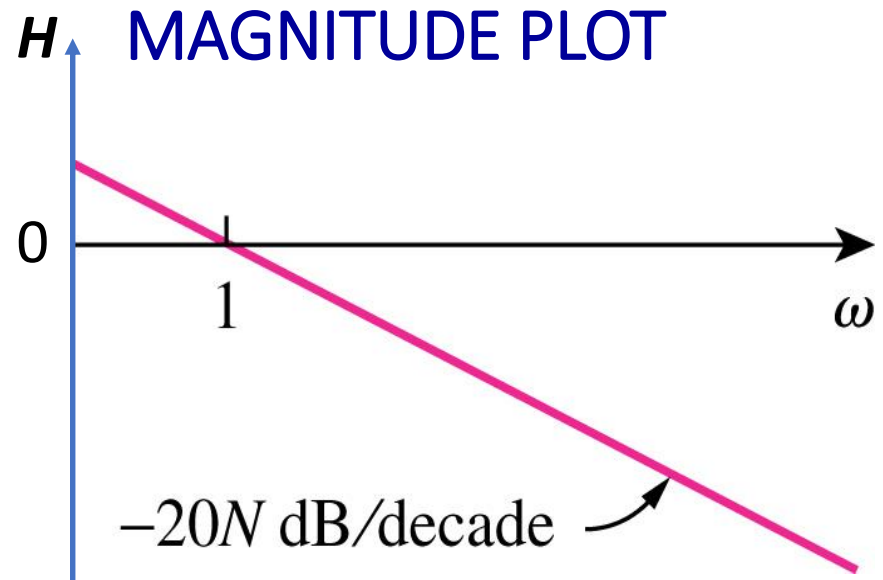

# BODE PLOT OF REAL ZERO or SIMPLE ZERO

## (4) REAL ZERO


$$H(\omega) = \frac{K(j\omega)^{\pm} (1 + j\omega/z_1) [(j\omega)^2 + 2\xi_1\omega_n + \omega_n^2]}{(1 + j\omega/p_1) [(j\omega)^2 + 2\xi_2\omega_n + \omega_n^2]}$$

# CHARACTERISTIC OF $(1+j\omega/z_1)^N$

- Magnitude:

$$H = \begin{cases} 0 & \omega < z_1 \\ 20N \text{ (dB/dec)} & \omega \geq z_1 \end{cases}$$


MAGNITUDE PLOT

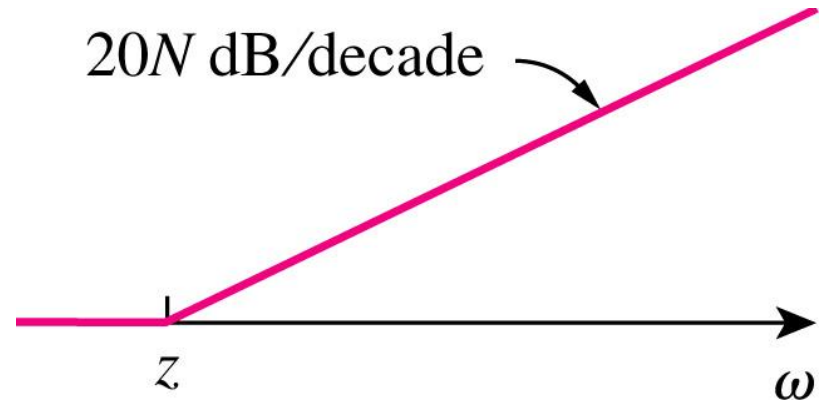

- Phase:

$$\phi = \begin{cases} 0 & \omega = 0 \\ 45^\circ & \omega = z_1 \\ 90^\circ & \omega \rightarrow \infty \end{cases}$$

PHASE PLOT

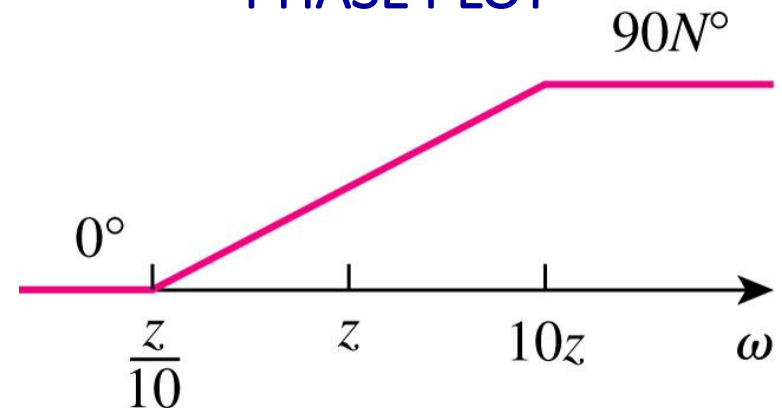




$$\mathbf{H}^{\text{simple\_zero}}(\omega) = (1 + j\omega/z_1)$$

$$\Rightarrow \begin{cases} H_{\text{dB}}^{\text{simple\_zero}} = 20 \log_{10} |1 + j\omega/z_1| \\ \phi = \tan^{-1} \frac{\omega}{z_1} \end{cases}$$


$$H_{\text{dB}}^{\text{simple\_zero}} = \begin{cases} 20 \log_{10} 1 = 0, & \omega \rightarrow 0 \\ 20 \log_{10} \frac{\omega}{z_1}, & \omega \rightarrow \infty \end{cases}; \quad \phi = \tan^{-1} \frac{\omega}{z_1} = \begin{cases} 0^\circ, & \omega \rightarrow 0 \\ 45^\circ, & \omega = z_1 \\ 90^\circ, & \omega \rightarrow \infty \end{cases}$$

## MAGNITUDE PLOT

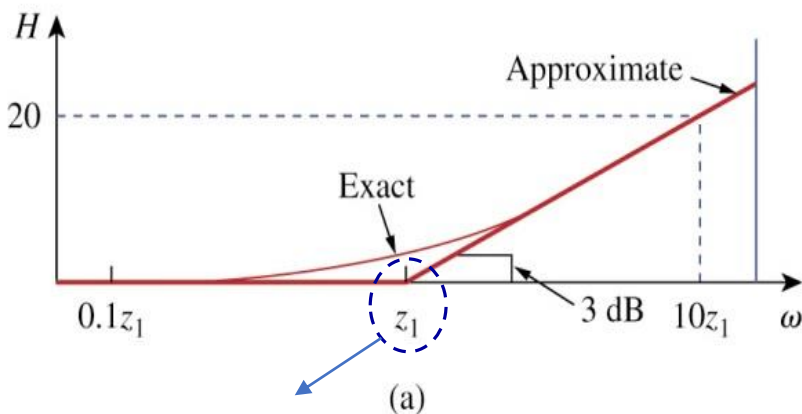

**Corner frequency/break frequency**

## PHASE PLOT

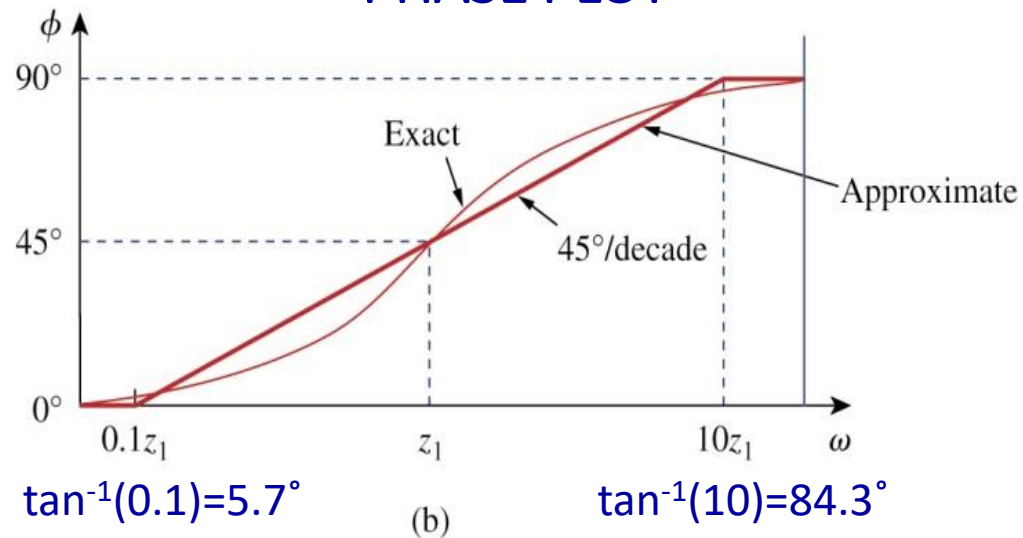

# BODE PLOT OF REAL POLE or SIMPLE POLE

## (5) REAL POLE

$$H(\omega) = \frac{K(j\omega)^{\pm} (1 + j\omega/z_1) [(j\omega)^2 + 2\xi_1\omega_n + \omega_n^2]}{(1 + j\omega/p_1) [(j\omega)^2 + 2\xi_2\omega_n + \omega_n^2]}$$

### Simple Pole


The Bode plots for the pole  $1/(1 + j\omega/p_1)$  are similar to those of the zero  $(1 + j\omega/z_1)$ , except that the corner frequency is at  $\omega = p_1$ , the magnitude has a slope of  $-20$  dB/decade, and the phase has a slope of  $-45^\circ$  per decade.

# CHARACTERISTIC OF $(1+j\omega/p_1)^{-N}$

- **Magnitude:**

$$H = \begin{cases} 0 & \omega < p_1 \\ -20N \text{ dB/dec} & \omega \geq p_1 \end{cases}$$


## MAGNITUDE PLOT

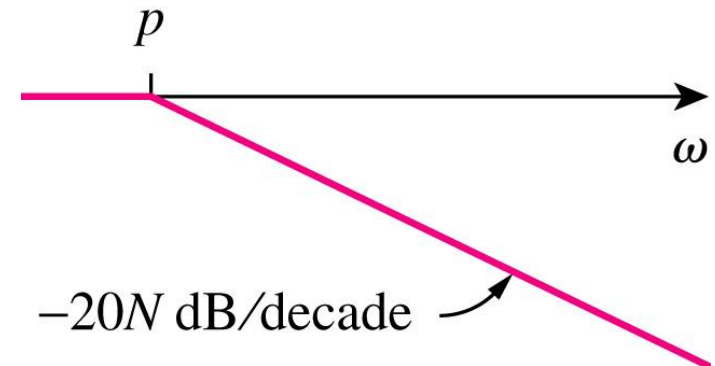

- **Phase:**

$$\phi = \begin{cases} 0 & \omega = 0 \\ -45^\circ & \omega = p_1 \\ -90^\circ & \omega \rightarrow \infty \end{cases}$$

## PHASE PLOT

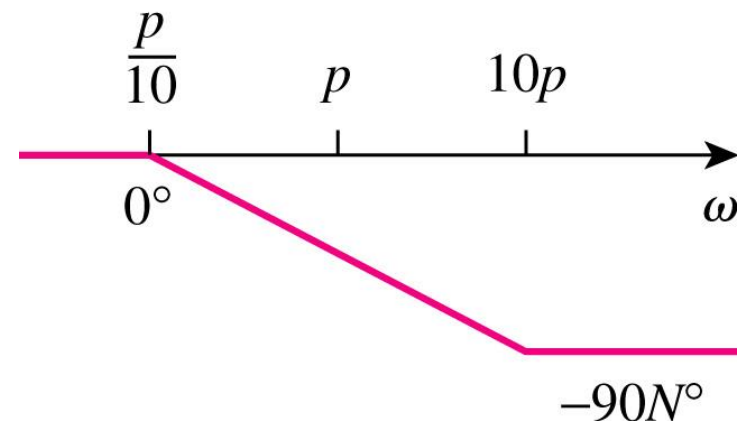

# (5) REAL POLE


## Magnitude

$$H_{dB} = 20 \log_{10} \left| \frac{1}{1 + j\omega / p_1} \right| = -20 \log_{10} |1 + j\omega / p_1|$$

$$\omega \rightarrow 0 \Rightarrow H_{dB} = -20 \log_{10} 1 = 0$$

$$\omega \rightarrow \infty \Rightarrow H_{dB} = -20 \log_{10} \omega / p_1$$

$$\omega = p_1 \Rightarrow H_{dB} = -20 \log_{10} |1 + j1| = -20 \log_{10} \sqrt{2} = -3$$

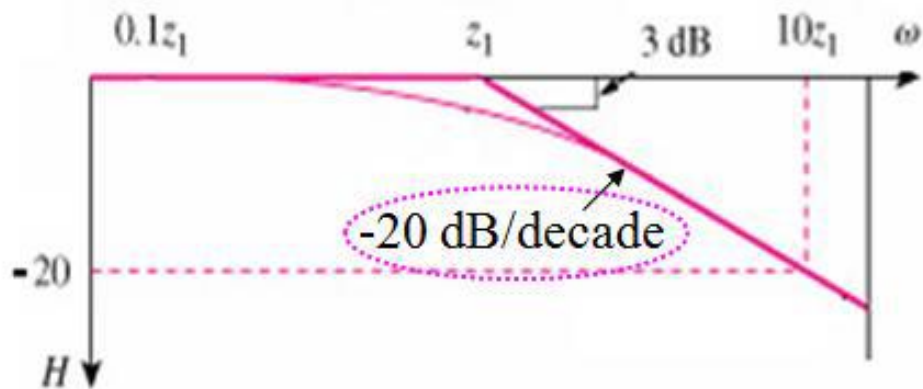

MAGNITUDE PLOT

## Phase


$$H(\omega) = \frac{1}{1 + j\omega / p_1}$$

$$\Rightarrow \phi(\omega) = -\tan^{-1}(\omega / p_1)$$

$$\phi(\omega \rightarrow 0) = 0$$

$$\phi(\omega \rightarrow \infty) = -90^\circ$$

$$\phi(\omega = z_1) = -45^\circ$$

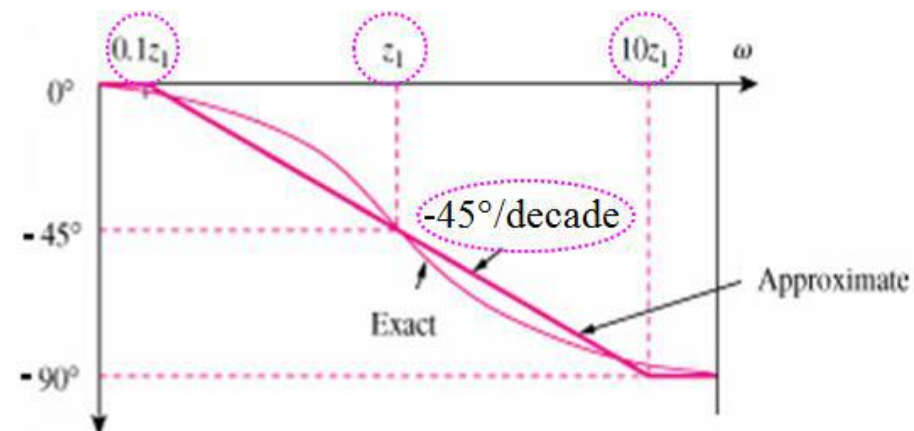

PHASE PLOT

# BODE PLOT OF QUADRATIC ZERO

## (6) QUADRATIC ZERO


$$H(\omega) = \frac{K(j\omega)^{\pm} (1 + j\omega/z_1) [(j\omega)^2 + 2\xi_1\omega_n + \omega_n^2]}{(1 + j\omega/p_1) [(j\omega)^2 + 2\xi_2\omega_n + \omega_n^2]}$$

# CHARACTERISTIC OF $(j\omega^2 + 2\xi\omega_n + \omega_n^2)^N$

- Magnitude:

$$H = \begin{cases} 0 & \omega < \omega_n \\ 40N \text{ dB/dec} & \omega \geq \omega_n \end{cases}$$


## MAGNITUDE PLOT

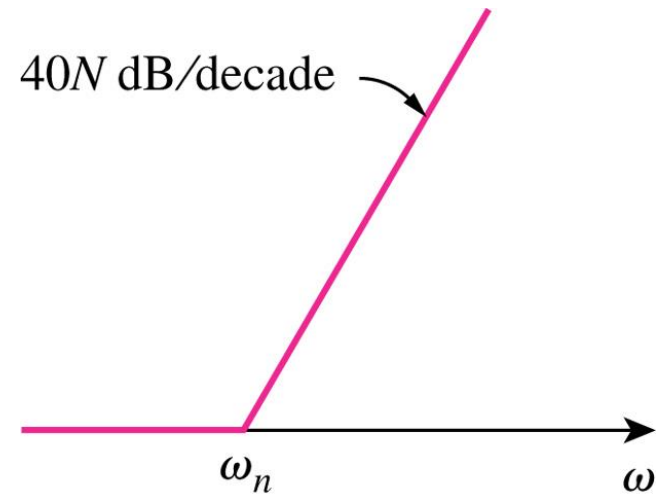

- Phase:

$$\phi = \begin{cases} 0 & \omega = 0 \\ 90^\circ & \omega = \omega_n \\ 180^\circ & \omega \rightarrow \infty \end{cases}$$



## PHASE PLOT

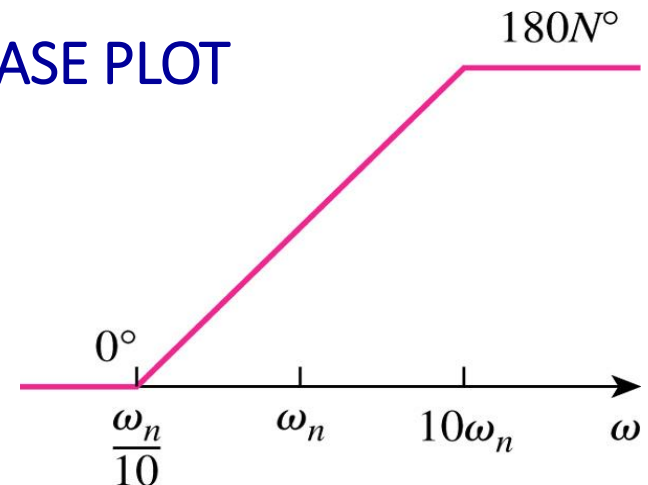

$$\mathbf{H}^{\text{quad\_zero}}(\omega) = 1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2 \quad (\text{complex poles for } \zeta_2 < 1)$$

$$\Rightarrow \left\{ \begin{array}{l} H_{\text{dB}}^{\text{quad\_zero}} = 20\log_{10} \left| 1 + \frac{j2\zeta_1\omega}{\omega_k} + \left( \frac{j\omega}{\omega_k} \right)^2 \right| \\ \phi = \tan^{-1} \frac{2\zeta_1\omega/\omega_k}{1 - \omega^2/\omega_k^2} \end{array} \right.$$
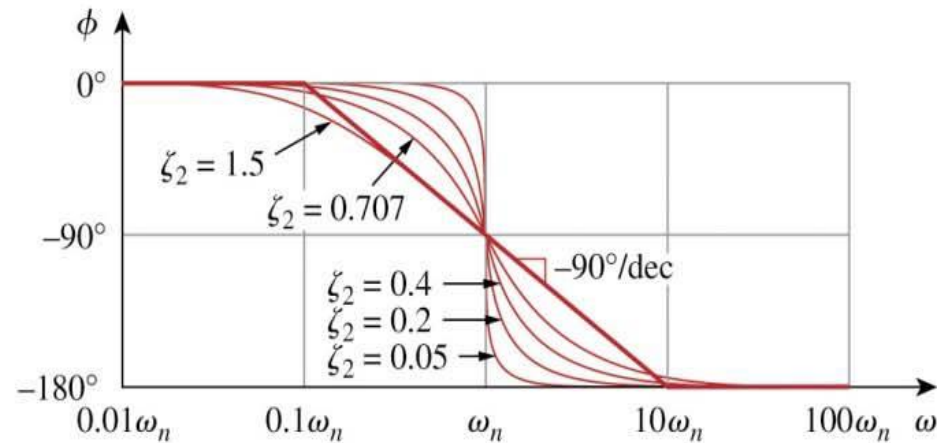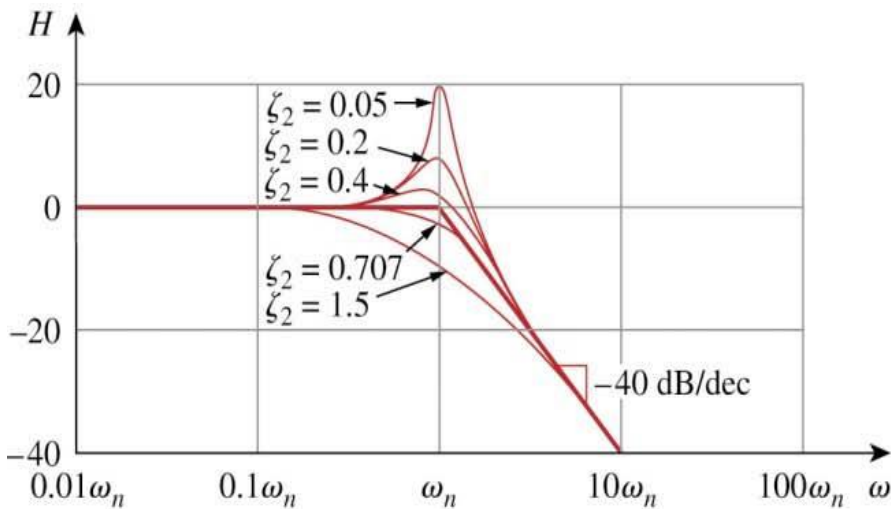
$$\Rightarrow H_{\text{dB}}^{\text{quad\_zero}} = \begin{cases} 0, & \omega \rightarrow 0 \\ 40\log_{10} \frac{\omega}{\omega_k}, & \omega \rightarrow \infty \end{cases}; \phi = \tan^{-1} \frac{2\zeta_1\omega/\omega_k}{1 - \omega^2/\omega_k^2} = \begin{cases} 0, & \omega = 0 \\ 90^\circ, & \omega = \omega_k \\ 180^\circ, & \omega \rightarrow \infty \end{cases}$$



# BODE PLOT OF QUADRATIC POLE

## (7) QUADRATIC POLE

$$H(\omega) = \frac{K(j\omega)^{\pm} (1 + j\omega/z_1) [(j\omega)^2 + 2\xi_1\omega_n + \omega_n^2]}{(1 + j\omega/p_1) [(j\omega)^2 + 2\xi_2\omega_n + \omega_n^2]}$$




# CHARACTERISTIC OF $(j\omega^2+2\xi\omega_n+\omega_n^2)^{-N}$

## • Magnitude:


$$H = \begin{cases} 0 & \omega < \omega_n \\ -40N \text{ dB/dec} & \omega \geq \omega_n \end{cases}$$

## MAGNITUDE PLOT

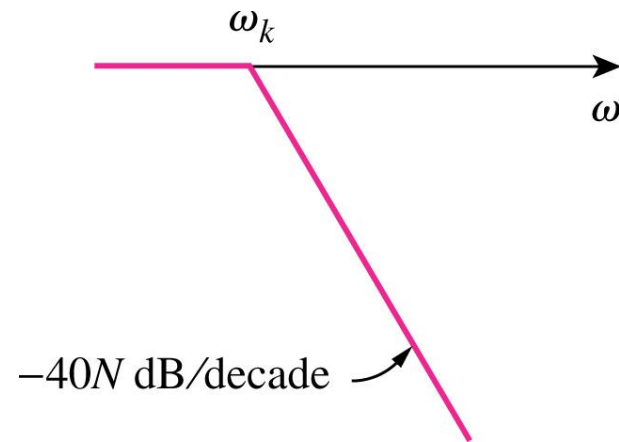
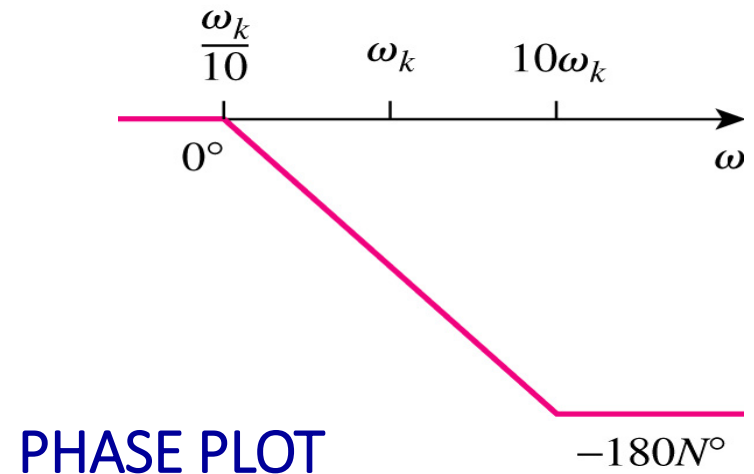
## • Phase:



$$\phi = \begin{cases} 0 & \omega = 0 \\ -90^\circ & \omega = \omega_n \\ -180^\circ & \omega \rightarrow \infty \end{cases}$$



$$\mathbf{H}^{\text{quad\_zero}}(\omega) = 1/\left(1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2\right) \quad (\text{complex poles for } \zeta_2 < 1)$$

$$\Rightarrow \left\{ \begin{array}{l} H_{\text{dB}}^{\text{quad\_zero}} = -20\log_{10} \left| 1 + \frac{j2\zeta_2\omega}{\omega_n} + \left( \frac{j\omega}{\omega_n} \right)^2 \right| \\ \phi = -\tan^{-1} \frac{2\zeta_2\omega/\omega_n}{1 - \omega^2/\omega_n^2} \end{array} \right.$$
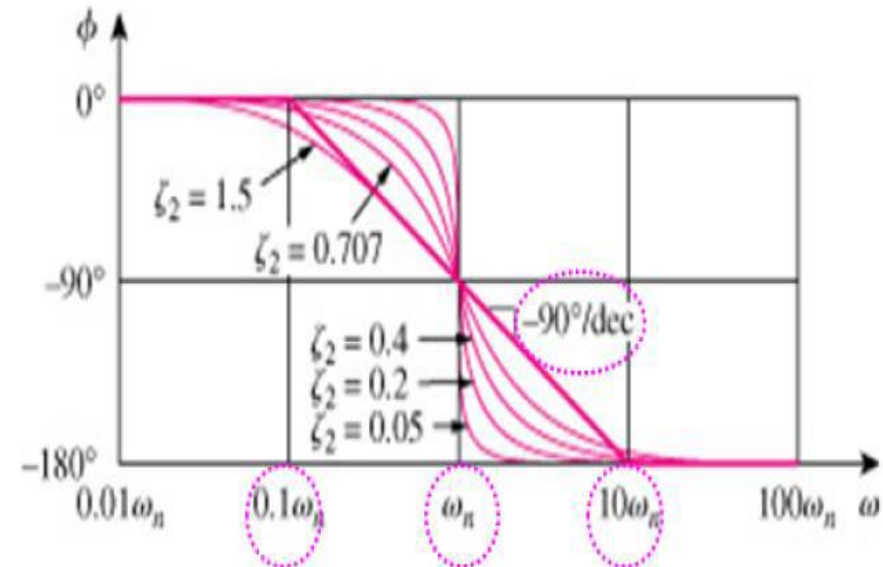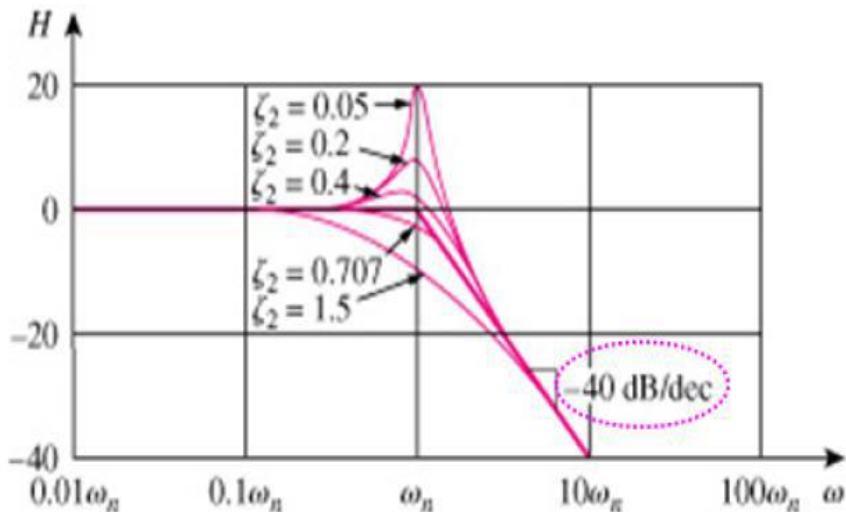
$$\Rightarrow H_{\text{dB}}^{\text{quad\_zero}} = \begin{cases} 0, & \omega \rightarrow 0 \\ -40\log_{10} \frac{\omega}{\omega_n}, & \omega \rightarrow \infty \end{cases}; \quad \phi = -\tan^{-1} \frac{2\zeta_2\omega/\omega_n}{1 - \omega^2/\omega_n^2} = \begin{cases} 0, & \omega = 0 \\ -90^\circ, & \omega = \omega_n \\ -180^\circ, & \omega \rightarrow \infty \end{cases}$$



# HOW TO DRAW A BODE PLOT

- While drawing the bode plot, every factor (i.e zeros/poles) were drawn separately on the semilog graph.
- Finally, all of the factor are combined to form the answer.

## EX.1

Draw the Bode plot for the given TF below:

$$H(\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)}$$

## SOLUTION

General equation:

$$\begin{aligned} H(\omega) &= \frac{200 j\omega}{(j\omega + 2)(j\omega + 10)} \\ &= \frac{200 j\omega}{(2)(1 + j\omega/2)(10)(1 + j\omega/10)} \\ &= \frac{10 j\omega}{(1 + j\omega/2)(1 + j\omega/10)} \end{aligned}$$

Magnitude of TF:

$$H_{dB} = 20 \log_{10} 10 + 20 \log_{10} |j\omega| - 20 \log_{10} \left| 1 + \frac{j\omega}{2} \right| - 20 \log_{10} \left| 1 + \frac{j\omega}{10} \right|$$




$20 \log 10 = 20\text{dB}$ : straight line

- Phase of TF:

$$\phi = 90^{\circ} - \tan^{-1} \frac{\omega}{2} - \tan^{-1} \frac{\omega}{10}$$

Zero at the origin

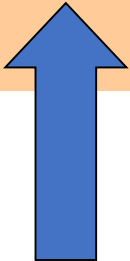








Pole at 2




Pole at 10



# MAGNITUDE PLOT GUIDANCE


	$\omega=0.1$	$\omega=2$	$\omega=10$	$\omega=100$
$z=0$	20dB/dec	20dB/dec 	20dB/dec 	20dB/dec 
$p=2$	0dB/dec	-20dB/dec	-20dB/dec	-20dB/dec
$p=10$	0dB/dec 	0dB/dec 	-20dB/dec 	-20dB/dec 
Resultant	=20dB/dec	=0dB/dec	=-20dB/dec	=-20dB/dec

# Magnitude plot

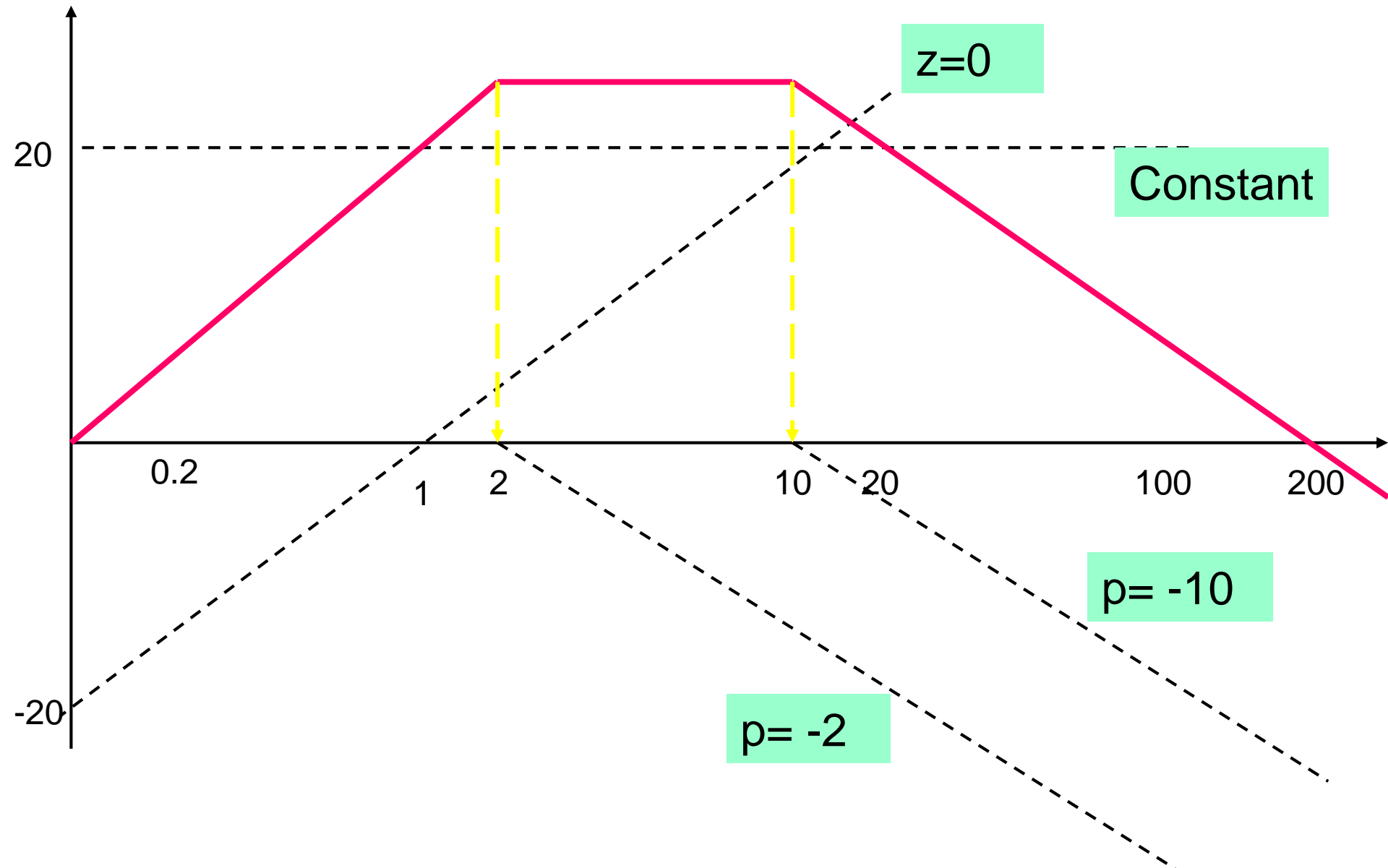



$$H_{dB} = 20\log_{10} 10 + 20\log_{10} |j\omega| - 20\log_{10} \left| 1 + \frac{j\omega}{2} \right| - 20\log_{10} \left| 1 + \frac{j\omega}{10} \right|$$

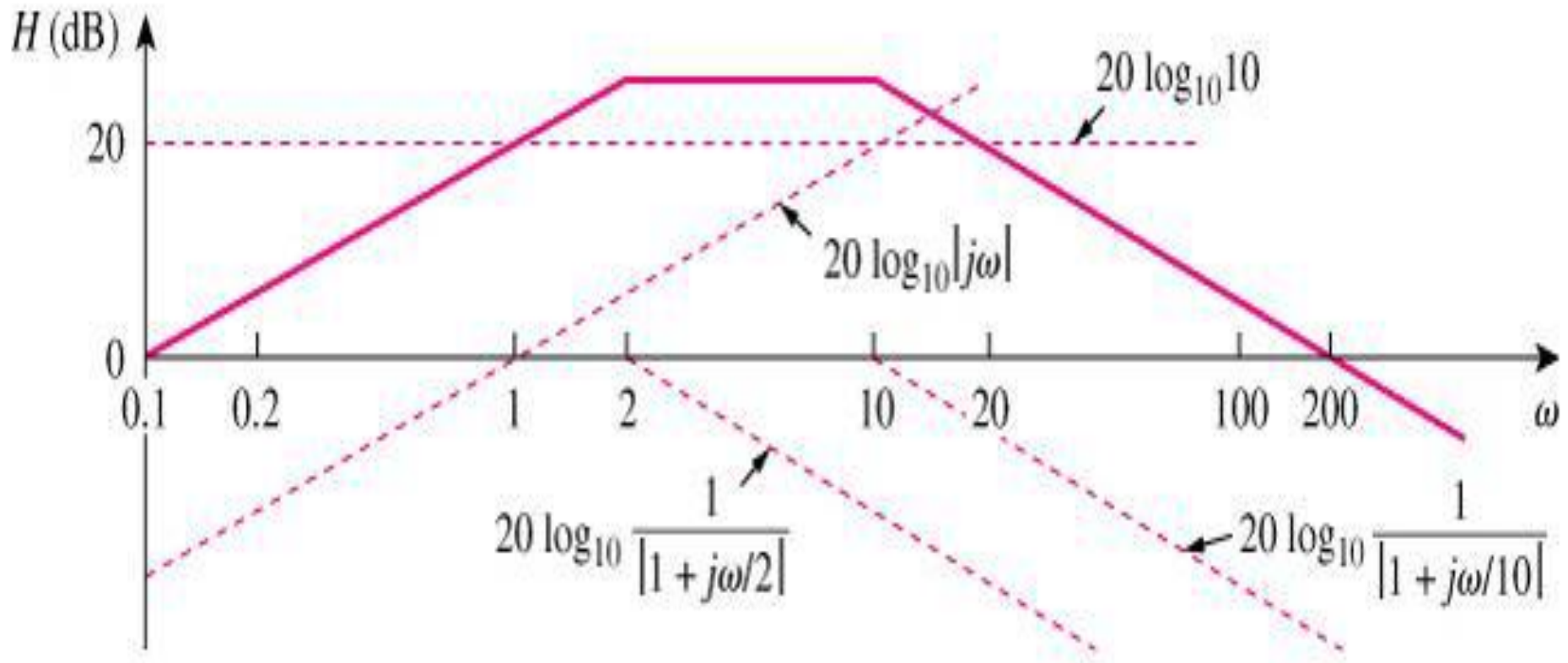



# PHASE PLOT GUIDANCE

	$\omega=0$	$\omega=0.2$	$\omega=1$	$\omega=20$	$\omega=100$
$z=0$	$90^\circ$	$90^\circ$	$90^\circ$	$90^\circ$	$90^\circ$
$p=2$	$0^\circ/\text{dec}$	$-45^\circ/\text{dec}$	$-45^\circ/\text{dec}$	$-90^\circ$	$-90^\circ$
$p=10$	$0^\circ/\text{dec}$	$0^\circ/\text{dec}$	$-45^\circ/\text{dec}$	$-45^\circ/\text{dec}$	$-90^\circ$
<b>Resultant</b>	$90^\circ$	$-45^\circ/\text{dec}$	$-90^\circ/\text{dec}$	$-45^\circ/\text{dec}$	$-90^\circ$

**Add all of the lines that having a slope only**

# Phase plot

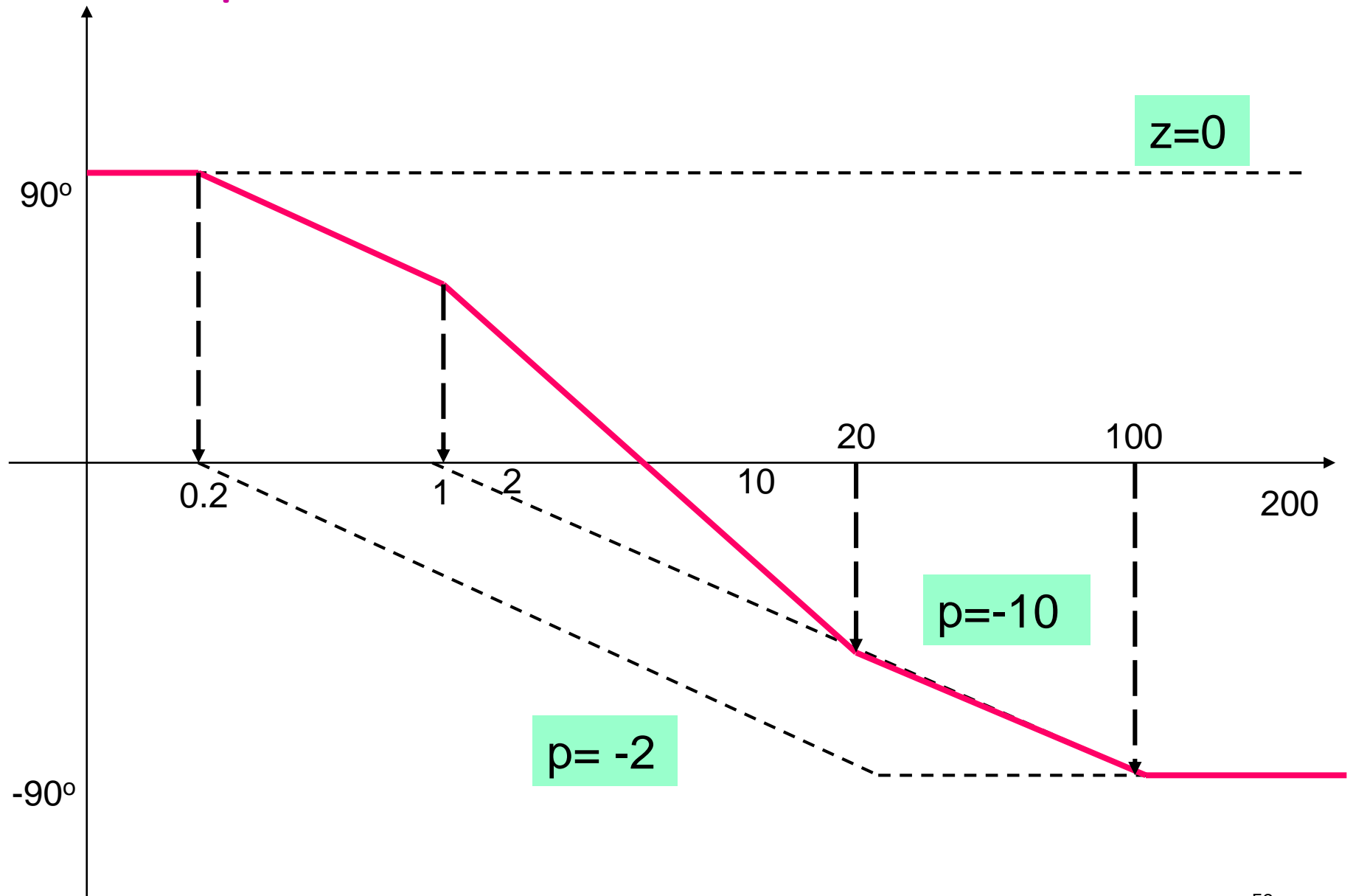

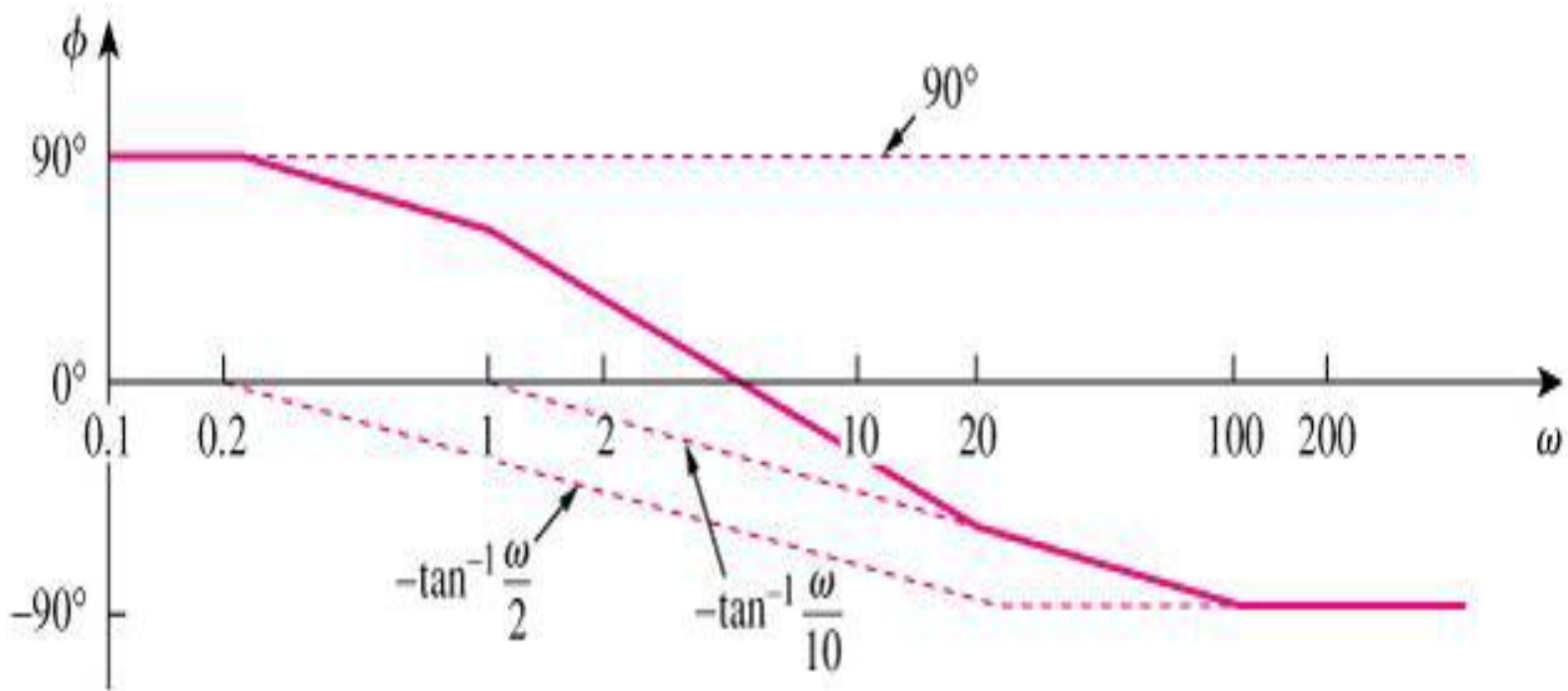

## EX.2

Draw the Bode plot for the given TF below:

$$H(\omega) = \frac{(j\omega + 10)}{j\omega(j\omega + 2)}$$

## SOLUTION

- General equation:

$$\begin{aligned} H(\omega) &= \frac{(j\omega + 10)}{j\omega(j\omega + 2)} \\ &= \frac{5(1 + j\omega/10)}{j\omega(1 + j\omega/2)} \end{aligned}$$


Magnitude of TF :


$$\begin{aligned} H_{dB} &= 20\log_{10} 5 + 20\log_{10} \left| 1 + \frac{j\omega}{10} \right| \\ &\quad - 20\log_{10} |j\omega| - 20\log_{10} \left| 1 + \frac{j\omega}{2} \right| \end{aligned}$$


$20 \log 5 = 14\text{dB}$  : straight line

- Phase of TF:



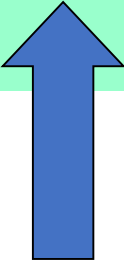
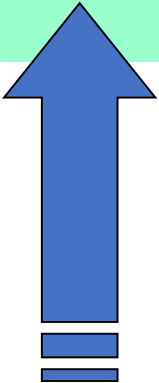
$$\phi = -90^{\circ} + \tan^{-1} \frac{\omega}{10} - \tan^{-1} \frac{\omega}{2}$$

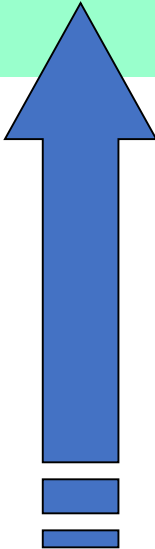
$$p_1=0$$


$$z_1 = -10$$

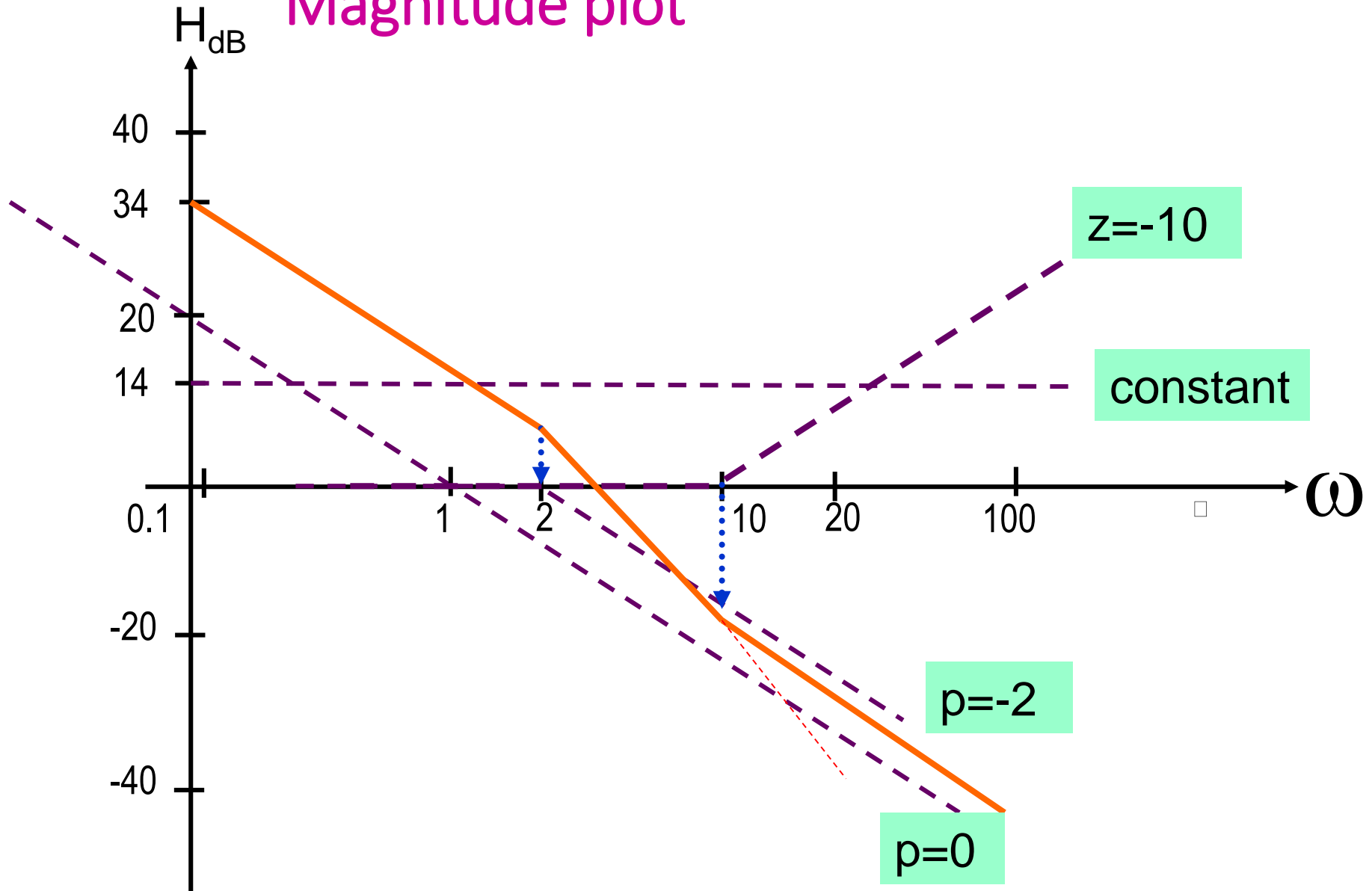

$$p_2 = -2$$

# MAGNITUDE PLOT GUIDANCE

	$\omega=0.1$	$\omega=2$	$\omega=10$	$\omega=100$
$p=0$	-20dB/dec	-20dB/dec	-20dB/dec	-20dB/dec
$p=2$	0dB/dec	-20dB/dec	-20dB/dec	-20dB/dec
$z=10$	0dB/dec 	0dB/dec 	20dB/dec 	20dB/dec 
Resultant	-20dB/dec	-40dB/dec	-20dB/dec	- 20dB/dec



# Magnitude plot




# Phase plot Guidance

	$\omega=0$	$\omega=0.2$	$\omega=1$	$\omega=20$	$\omega=100$
$p=0$	$-90^\circ$	$-90^\circ$	$-90^\circ$	$-90^\circ$	$-90^\circ$
$p=2$	$0^\circ/\text{dec}$	$-45^\circ/\text{dec}$	$-45^\circ/\text{dec}$	$-90^\circ$	$-90^\circ$
$z=10$	$0^\circ/\text{dec}$	$0^\circ/\text{dec}$	$45^\circ/\text{dec}$	$45^\circ/\text{dec}$	$90^\circ$
Resultant	$-90^\circ$	$-45^\circ/\text{dec}$	$0^\circ/\text{dec}$	$45^\circ/\text{dec}$	$-90^\circ$

Add all the lines that having a slope only

# Phase plot

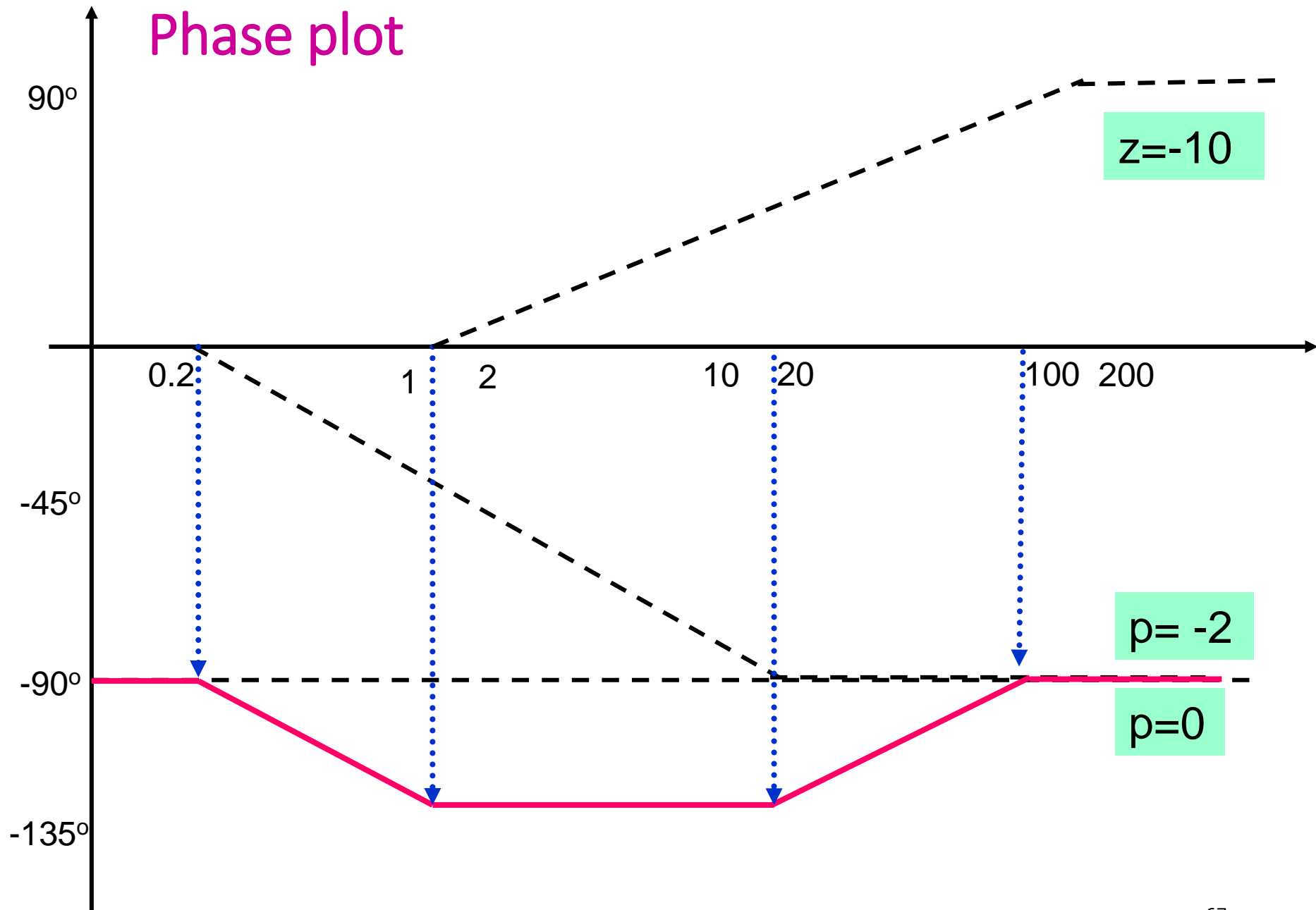

## EXAMPLE 3

- Draw the Bode plot for the given TF below:

$$H(s) = \frac{s}{s^2 + 10s + 100}$$

# SOLUTION

- Standard equation:

$$H(s) = \frac{s}{s^2 + 10s + 100}$$

Replace  $s = j\omega$  and divide it with 100;

$$\mathbf{H}(\omega) = \frac{j\omega}{100(1 + j\omega/10 - \omega^2/100)}$$


- Magnitude of TF:

$$\begin{aligned} H_{dB} = & 20\log_{10}|j\omega| - 20\log_{10}|100| \\ & - 20\log_{10}|1 + j\omega/10 - \omega^2/100| \end{aligned}$$


$$-20 \log 100 = -40\text{dB} : \text{straight line}$$

- Phase of TF:
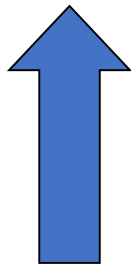
$$\phi = 90^\circ - \tan^{-1} \left( \frac{\omega/10}{1 - \omega^2/100} \right)$$




$$z_1 = 0$$

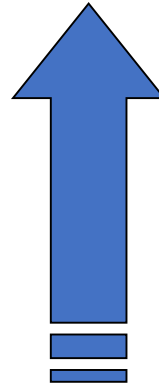


$$\omega_n = 10$$

# Magnitude plot

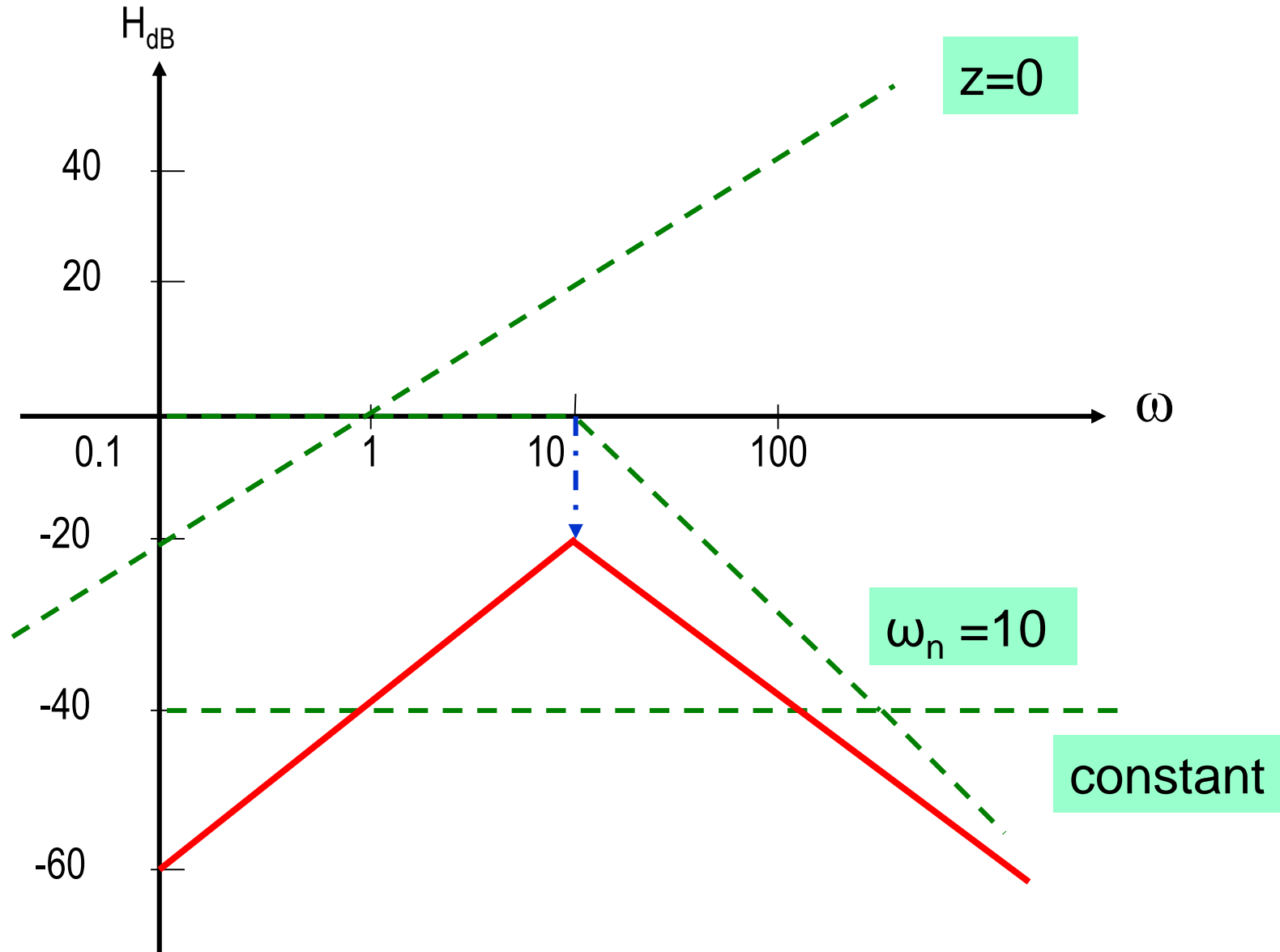


# Phase plot

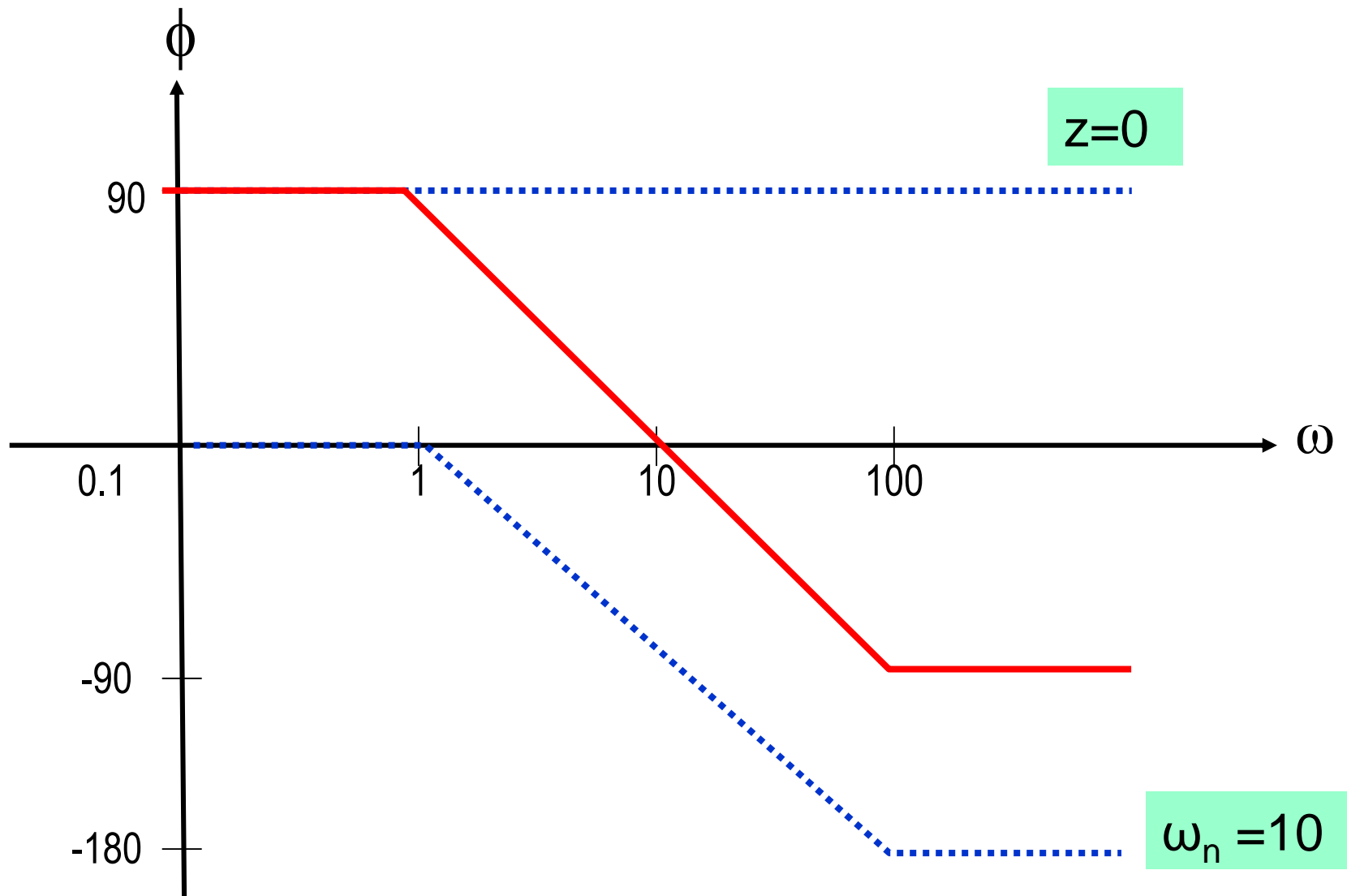



## EXAMPLE 4

- Determine the TF ?

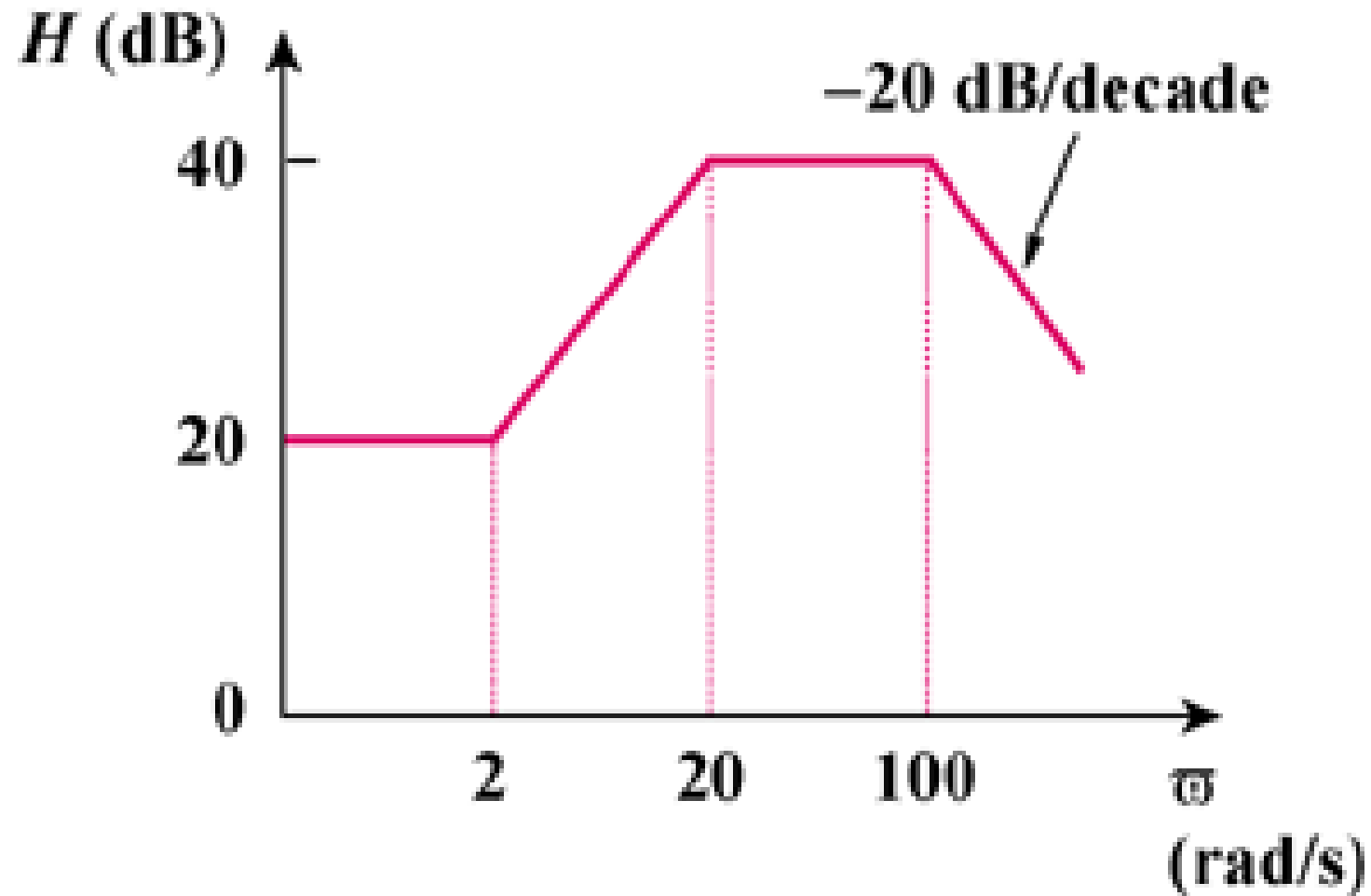

ANSWER

$$\mathbf{H(\omega) = \frac{10^4 (2 + j\omega)}{(20 + j\omega)(100 + j\omega)}}$$